

**The George Washington University
School of Engineering and Applied Science
Department of Electrical and Computer Engineering
ECE 20 - LAB
Experiment # 4**

Characterization of an NPN Bipolar Junction Transistor (BJT)

Components:

Kit Part #	Spice Part Name	Part Description	Symbol Name (used in schematics throughout this lab manual)
2N3904	Q2N3904	NPN Bipolar Junction Transistor (BJT)	Q1
Resistor	R	100kΩ Resistor	RB
Resistor	R	1kΩ Resistor	RC

Table 1.1

Objectives:

- To characterize a BJT using the Tektronix Model 571 Curve Tracer
- To characterize the base-emitter pn-junction (BEJ) and base-collector pn-junction (BCJ) of a BJT using the Tektronix Model 571 Curve Tracer
- To characterize a BJT using a Power Supply & Keithley Model 175 DMM
- To compare measured characterization results to manufacturer specifications

Prelab: (*Submit electronically prior to lab meeting, also have a printed copy for yourself during lab*)

1. Read through lab, generate an equipment list.
2. Create a table called: Table P.1 with the following cell headings:

Calculated Values					Simulated Values					Measured Values						
I_B	V_{CE}	I_C	V_{BE}	β	I_B	V_{CE}	I_C	V_{BE}	β	I_B	V_{CC}	V_{CE}	I_C	V_{BB}	V_{BE}	β

3. Build & simulate the circuit in figure P.1 using SPICE
 - a) Using the “Parametric Sweep Simulation of a BJT” SPICE tutorial on the lab website to generate an IV Curve (I_C vs V_{CE}) for the 2N3904 BJT transistor:
 - b) Sweep V_{CE} from 0 to 10V, in .2V increments
 - c) Set I_B to be the “parameter” and step it from 10μ to $50\mu A$ in $20\mu A$ steps
 - d) Use a current probe to plot I_C vs. V_{CE} at each step of I_B to generate 3 curves
 - e) Place markers at $V_{CE}=2V$ on each curve
 - f) Record the values for: V_{CE} , I_C , and I_B from the curve markers in Table P.1, the values for V_{BE} will be found in step i)
 - g) Delete the I_C current probe & place a voltage probe at node V_B as shown in fig P.2
 - h) Re-run the same simulation, place markers at $V_{CE}=2V$ on each curve
 - i) Record the values for: V_{BE} , from the curve markers in Table P.1
 - j) Calculate the value of the DC current gain ($\beta = I_C / I_B$) for each row of table P.1

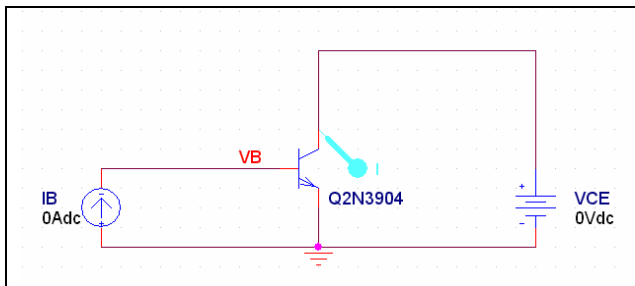


Figure P.1- Circuit to generate I_C vs. V_{CE} curve (I_B curves)

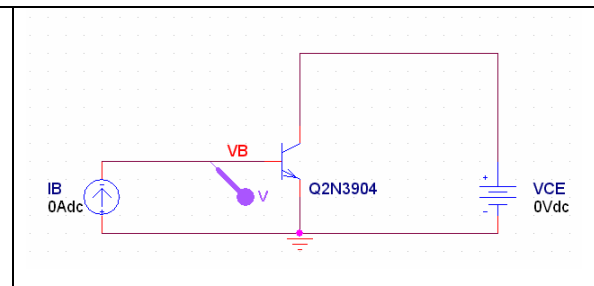


Figure P.2 Circuit to generate I_C vs. V_{CE} curve (V_{BE} curves)

4. Use equation P.1 to calculate I_C and record the values in the “calculated value” section of table P.1
 - a) Calculate I_C for each value of V_{BE} collected in step 3
 - b) Assume $I_S=6.734\text{fA}$, and the typical value for $V_T \approx 26\text{mV}$ (thermal voltage)
 - c) Calculate the value of the DC current gain ($\beta = I_C / I_B$) for each row of table P.1

$$I_C \cong I_S \left(e^{\frac{V_{BE}}{V_T}} \right)$$

Equation P.1 – Collector Current of NPN BJT in the active region of operation (Assumptions: $V_A \gg V_{CE}$ and $n=1$)

5. In the simulation above, we have swept V_{CE} from 0 to 10V, and I_B from 10μ to $50\mu\text{A}$. But the 2N3904 BJT can handle a significantly higher set of values. From the specification sheet for the 2N3904 BJT, gather the following specifications:

Parameter	Value (with units)
Maximum Collector-Emitter Voltage (V_{CEO})	
Maximum Emitter-Base Voltage (V_{EBO})	
Maximum Continuous Collector Current (I_C)	
Maximum Collector-Base Voltage (V_{CBO})	
Maximum DC Current Gain (β or h_{FE})	
Base-Emitter ON Voltage (V_{BE}) when $V_{CE}=5\text{V}$ and $I_C=10\text{mA}$ at room temperature (note: see graph section of spec)	

LAB:

Part I – Transistor Characterization using a Curve Tracer:

Generating an I_C vs. V_{CE} IV-Curve for the BJT:

- a. Allow the GTA to demonstrate using the Tektronix Model 571 Curve Tracer for an NPN device.
- b. Set the Tektronix Model 571 Curve Tracer to generate 3 IV-curves for the 2N3904 Transistor with the following limits:
 - Limit I_C to be no greater than 10mA
 - Set V_{CE} to be swept from 0 to 10V
 - Step I_B from 10μ to $50\mu A$ in $20\mu A$ steps to generate the 3 curves
 - Print the resulting family of curves, annotate I_B on each curve (by hand), and indicate the limits of your setup in the lab write-up. Be sure to scan the printout into your lab write-up.

Generating the IV-Curve for BEJ and CEJ for the BJT pn-junctions:

- c. Set the Tektronix Model 571 Curve Tracer to generate the forward IV characteristic curve for the Base-Emitter Junction of the 2N3904 Transistor.
 - Determine the limits for the B-E junction using the manufacturer specification sheet as done in lab 1
 - Print the resulting curve, indicate the voltage & current limits and scan the printout into your lab write-up
- d. Set the Tektronix Model 571 Curve Tracer to generate the forward IV characteristic curve for the Base-Collector Junction of the 2N3904 Transistor.
 - Determine the limits for the B-E junction using the manufacturer specification sheet as done in lab 1
 - Print the resulting curve, indicate the voltage & current limits and scan the printout into your lab write-up

Part II – Transistor Characterization Using a Test Circuit - Generating the I_C vs. V_{CE} family of IV-Curves for a BJT:

In this lab, you will generate only 3 IV-Curves (I_C vs. V_{CE}) as you did in the prelab. I_B will be the 'parameter' whose value will step from $I_B=10\mu A$ to $50\mu A$ in $20\mu A$ steps.

In the prelab you generated an IV-Curve for the 2N3904 using the schematic in figure P.1. You were able to generate base current I_B in the range of 0 to $50\mu A$. In the lab, the power supply can behave as a current source, but it cannot produce a current as small as $50\mu A$. To create the same family of IV-Curve in the lab, we must use the circuit in figure L.1. The voltage source combined with the $100k\Omega$ resistor at the base will behave as the 0 to $50\mu A$ current source from figure P.1.

The data collected during this section of lab is to be recorded under the "Measured Values" section of Table P.1

Measuring the $I_B=10\mu A$ curve

- Build the circuit depicted in figure L.1 using the 2N3904 BJT
- Measure the exact resistance of R_B using the Ohm meter, record this value
- Measure the exact resistance of R_C using the Ohm meter, record this value
- Use a DMM to measure the voltage at node V_B in the circuit L.1, this is V_{BE}
- Use a DMM to measure the voltage at node V_C in the circuit L.1, this is V_{CE}
- Adjust V_{CC} until V_{CE} equals 2V
- Adjust V_{BB} until V_{BE} equals the value found in prelab when $I_B=10\mu A$ & $V_{CE}=2V$
- Now, readjust V_{CC} until V_{CE} equals 0 V
- Record V_{CC} , V_{CE} , V_{BB} , & V_{BE} in table P.1
- Calculate the voltage across R_B to calculate and record current I_B in table P.1
- Calculate the voltage across R_C to calculate and record current I_C in table P.1
- Adjust V_{CE} from 0V to 2V in .2V steps, repeating steps (i)-(k) at each step
- Adjust V_{CE} from 2V to 10V in 1V steps, repeating steps (i)-(k) at each step.
- Calculate β for each recorded value of I_C and I_B

Measuring the $I_B=30\mu A$ curve

- Repeat steps (a)-(n) above, but in step (g) adjust V_{BB} until $I_B=30\mu A$; you will need to calculate the current I_B from the voltage across R_B .

Measuring the $I_B=50\mu A$ curve

- Repeat steps (a)-(n) above, but in step (g) adjust V_{BB} until $I_B=50\mu A$; you will need to calculate the current I_B from the voltage across R_B .

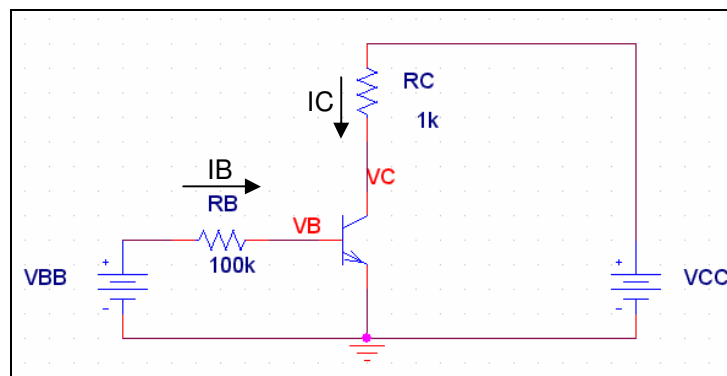


Figure L.1 – Test circuit to generate family of IV-curves for an NPN BJT

Part III – Data Analysis

1. Plot a family of IV-Curves for the data collected for *Calculated Values & Measured Values*, in table P.1
2. Extract a few values for IB, VCE, IC, and VBE from the curve-tracer plots, place these in another set of columns in table P.1
3. Compare the Calculated, Simulated, Measured (curve-tracer & Keithley measured values) via graphs (overlying them where possible) and percentage error in all cases.