

**The George Washington University
School of Engineering and Applied Science
Department of Electrical and Computer Engineering
ECE 20 - LAB
Experiment # 7**

Designing and Measuring a Common-Collector (Emitter-Follower) Amplifier

Components:

Kit Part #	Spice Part Name	Part Description	Symbol Name (used in schematics throughout this lab manual)
2N3904	Q2N3904	NPN Bipolar Junction Transistor (BJT)	Q1
Resistor	R	To be determined in prelab	R1
Resistor	R	To be determined in prelab	R2
Resistor	R	To be determined in prelab	RE

Table 1.1

Objectives:

- To design a common-collector amplifier to meet a set of specifications
- To simulate the designed common-collector amplifier
- To build the designed common-collector amplifier
- Measure Voltage gain (A_v) and Current gain (A_i) with and without load in laboratory
- Measure R_{in} , R_{out} with and without load in laboratory

Prelab: (*Submit electronically prior to lab meeting, also have a printed copy for yourself during lab*)

1. Read through lab, generate an equipment list.
2. Read the tutorial "Designing a Common-Collector Amplifier" for help.
3. Design a common-collector amplifier using a 2N3904 NPN BJT to meet the following specs (hand in all calculations):

Specification	Value
Quiescent Current (I_{cQ})	1mA
VCC	20V
A_v	1 V/V
R_{in} (DC)	70k Ω
RL	510 Ω
v_{in}	10mV @ 10kHz

- a) Using hand calculations, determine the current gain (A_i) for the amplifier without any load.
 - b) Using hand calculations, determine the input impedance (R_{IN}) for the amplifier without any load.
 - c) Using hand calculations, determine the output impedance (R_{OUT}) for the amplifier without any load.
4. Build the amplifier you've designed in SPICE, use 50 ohms for R_{sig} . Attach a 100meg load resistor to simulate an 'unloaded' amplifier.
 5. Perform a Bias Point Analysis for the circuit.
 6. Show the DC **voltages** and DC **currents** at each node; submit a separate screenshot for each. Verify that the DC currents and node voltage approximate your calculations.
 7. Perform a Transient Analysis, show 5 cycles of V_{in} (NOT V_{sig}) and V_{out} (with and without any load). Ensure that V_{in} and V_{out} are plotted in sub-windows, as done in lab 5. Place a label at the peak of V_{in} and V_{out} ; make sure to mark this at the same point in time.
 - a) Determine the small signal voltage gain of the amplifier (A_v) with load and without load. Verify that it approximates your calculations.
 - b) Increase V_{in} until V_{out} is distorted (looks like a clipped sine wave). What is the maximum value of V_{in} just as V_{out} is clipped? Does it match you calculated max

voltage swing from your IV-Curve for the 2N3904 transistor? Reset V_{in} to 10mV for the remainder of the simulations below.

8. Perform a Transient Analysis, show 5 cycles of I_n and I_{out} (with and then without any load). Ensure that I_n and I_{out} are plotted in sub-windows, as done in lab 5. Place a label at the peak of I_n and I_{out} ; make sure to mark this at the same point in time.
 - a) Determine the small signal current gain of the amplifier (A_i) with load and without load. Verify that it approximates your calculations.
9. Perform a Transient Analysis, show 5 cycles of V_{in} and I_n (with and then without any load). Ensure that V_{in} and I_n are plotted in sub-windows, as done in lab 5. Place a label at the peak of V_{in} and I_n ; make sure to mark this at the same point in time.
 - a) $R_{in}(AC) = V_{in} / I_n$, determine $R_{in}(AC)$ with and without load, verify that it approximates your calculations.
10. Perform a Transient Analysis, show 5 cycles of V_{out} and I_{out} (with and then without any load). Ensure that V_{out} and I_{out} are plotted in sub-windows, as done in lab 5. Place a label at the peak of V_{out} and I_{out} ; make sure to mark this at the same point in time.
 - a) $R_{out}(AC) = V_{out} / I_{out}$, determine $R_{out}(AC)$ with and without load, verify that it approximates your calculations.


Lab:

Part 1 - Bias Point Verification (Large signal measurements)

1. Measure ALL resistor using the Keithley 175 DMM prior to building the circuit
2. Construct the common emitter amplifier designed in the prelab.
3. **BEFORE** attaching the function generator + scope:
 - a. Measure V_B , V_E , V_C using the Keithley 175 DMM
 - b. From the measured voltages, calculate V_{BE} , V_{CE} , & V_{CB} , I_B , I_E , I_C , β
4. Place all hand calculated, simulated, and measured values for I_B , I_E , I_C , V_B , V_E , V_C , V_{BE} , V_{CE} , & V_{CB} in a single table for analysis in your lab writeup.

Part 2 - Common Collector Amplifier Measurement (Small signal measurements)

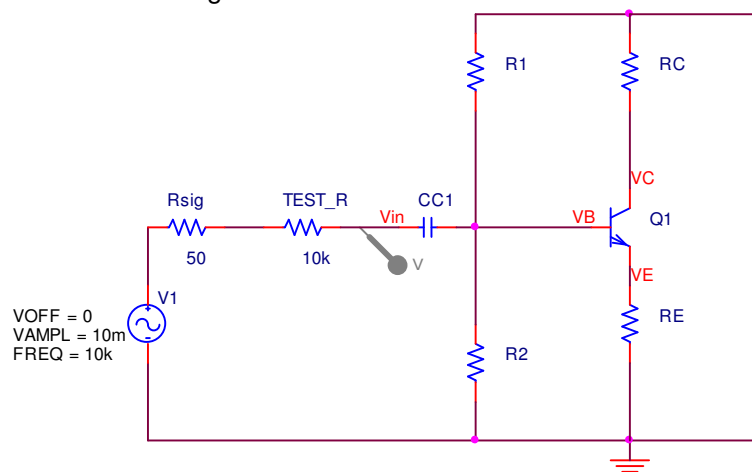1. Remove the 510 Ohm "load" from your amplifier
2. Apply the 10mV, 10kHz input signal using the function generator
 - Note: the 10mV set on the function generator is " v_{sig} ," NOT " v_{in} "
 - Note: the output impedance of the function generator is 50Ω , this is "Rsig"
3. Use Channel 1 of the digital oscilloscope to measure v_{in}
 - You CANNOT use autose. Determine the proper period for the 10kHz signal
 - Ensure channel 1 is set for AC coupling
 - On the scope, setup a "filter" (see vertical menu) for CH 1, to remove any noise
4. Use Channel 2 of the digital oscilloscope to measure v_{out}
 - You CANNOT use autose. Determine the proper period for the 10kHz signal
 - Ensure channel 2 is set for AC coupling
 - On the scope, setup a "filter" (see vertical menu) for CH 2, to remove any noise
5. You may add a large capacitor between VCC and GND to remove any additional noise in the circuit
6. Measure v_{out} , v_{in} with NO load; determine A_{v0} (no load)
7. Measure v_{out} , v_{in} with load; determine A_v
8. Use the following procedure to measure $R_{in} = v_{in} / I_{in}$
 - a. Remove the load resistor
 - b. Because the scope can only measure Voltage (not current), we use the following technique to determine R_{in} :
 - You have previously recorded v_{in} (unloaded)
 - Attach a $10k\Omega$ resistor in-between the function generator & your amplifier's input, measure the voltage across it



- Use Ohm's law to calculate the current through the $10k\Omega$ resistor, this is " I_{in} "
- Since the $10k\Omega$ is in series with your amplifier, " I_{in} " is the same with or without the $10k\Omega$ resistor
- Calculate $R_{in} = v_{in} / I_{in}$ (use the value for V_{in} recorded BEFORE the $10k\Omega$)

9. Increase V_{in} until V_{out} saturates/clips, record the value of V_{in} where saturation occurs
10. Calculate A_i (loaded and unloaded)
11. Calculate $R_{out} = V_{out} / I_{out}$ (loaded and unloaded)

Analysis / Writeup

- Include all hand calculations in the final lab writeup.
- For each part of the lab, create tables to compare your hand calculated data, simulated data, and measured data. If there are waveforms, reprint the waveforms from your prelab in your lab report, to accurately compare them to the waveforms captured in lab.
- Calculate % error of difference between hand calculations, simulations, and measurements.
- What is the maximum output voltage swing of your amplifier (Part II – Step 9)?
 - Did it match your calculations?
- Is the input impedance (R_{in}) of a common emitter amplifier high or low?
- Is the output impedance (R_{out}) of a common emitter amplifier high or low?
- Is the voltage gain load dependent?
- Is the common-collector amplifier suitable for small or large loads?