

**The George Washington University**  
**School of Engineering and Applied Science**  
**Department of Electrical and Computer Engineering**  
**ECE 20 - LAB**


**Experiment # 11**  
*MOSFET Amplifiers testing and designing*

**Equipment:**

You must make up a complete equipment list and have your instructor review it before you start.

**Objectives:**

- To verify the operating point for a MOSFET biasing network
- To verify the small signal performance for a given CSC amplifier:  $R_{IN}$ ,  $R_{OUT}$ ,  $A_v$ ,  $A_i$ , maximum input amplitude without distortion  $V_{in\ max}$ , etc.
- To verify the small signal performance for a given CDC amplifier:  $R_{IN}$ ,  $R_{OUT}$ ,  $A_v$ ,  $A_i$ , maximum input amplitude without distortion  $V_{in\ max}$ , etc.
- To establish the relationship between the voltage gain and the load

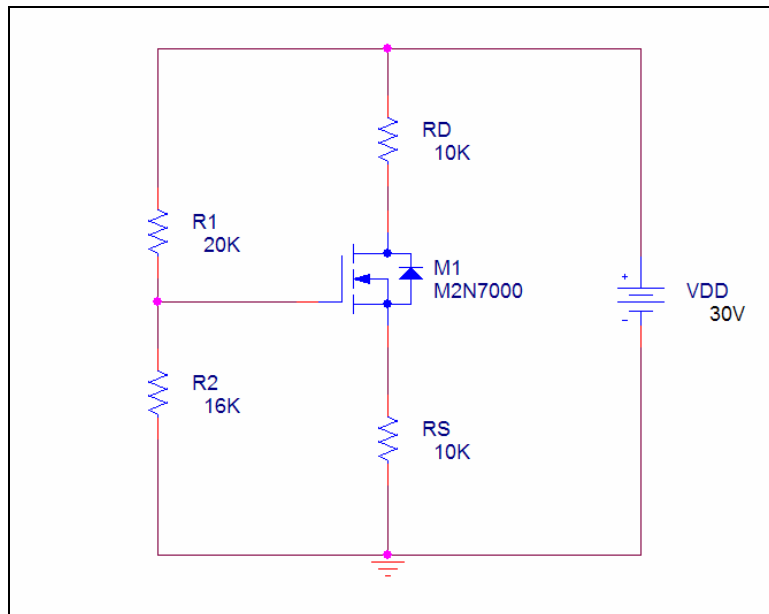

**Figure # 1 – DC Biased MOSFET**

## **1.- (HW) Analysis**

- a. Analyze the circuit shown in Figure # 1 (use nominal values) and find VGG, VG, VS, VD, and ID

(assume  $V_{DD} = 30$  Volts DC,  $K = 64$  mAmp/Volt<sup>2</sup>,  $V_{th} = 1.73$  V).

**note:**  $K = k_n'$  (W/L)

- b. Assemble this circuit on SPICE

-For M1, use Part: M2N7000 (**note:** the student edition doesn't include this part)

-Analysis Type: Bias Type

-Show the DC Node Voltages and Currents, to verify your calculations


## **2.- Verification**

- a. Build and fully test the circuit shown in Figure #1. Measure VG, VS, VD, and ID using the DMM.

### 3.- (HW) Analysis

Figure #1 can be configured as a CSC or CDC Amplifier. The DC Bias voltages and current remain the same as in Part 1 of this lab. Using the DC Bias Voltages & Currents that you have found, analyze the two different Amplifier Configurations below:

1. Refer to Figure #2 which shows the CSC configuration of the amplifier:
  - a. Find  $R_{OUT}$ ,  $R_{IN}$ ,  $A_{vo}$ ,  $A_v$  (set  $R_L=R_{OUT}$ ) and  $A_i$  (set  $R_L=R_{OUT}$ ).
  - b. Also, find the maximum input voltage ( $V_{in\ max}$ ) that the amplifier can accept before the output distorts (loaded and unloaded).
  
2. Create Figure #3, which connects Figure #1 in the CDC configuration.
  - a. Use a “shorting capacitor”  $CS$ , as was done in Figure #2, to short  $R_D$ .
  - b. Find  $R_{OUT}$ ,  $R_{IN}$ ,  $A_{vo}$ ,  $A_v$  ( $R_L=R_{OUT}$ ) and  $A_i$  ( $R_L=R_{OUT}$ ).
  - c. Also, find the maximum input voltage ( $V_{in\ max}$ ) that the amplifier can accept before the output distorts (loaded and unloaded).

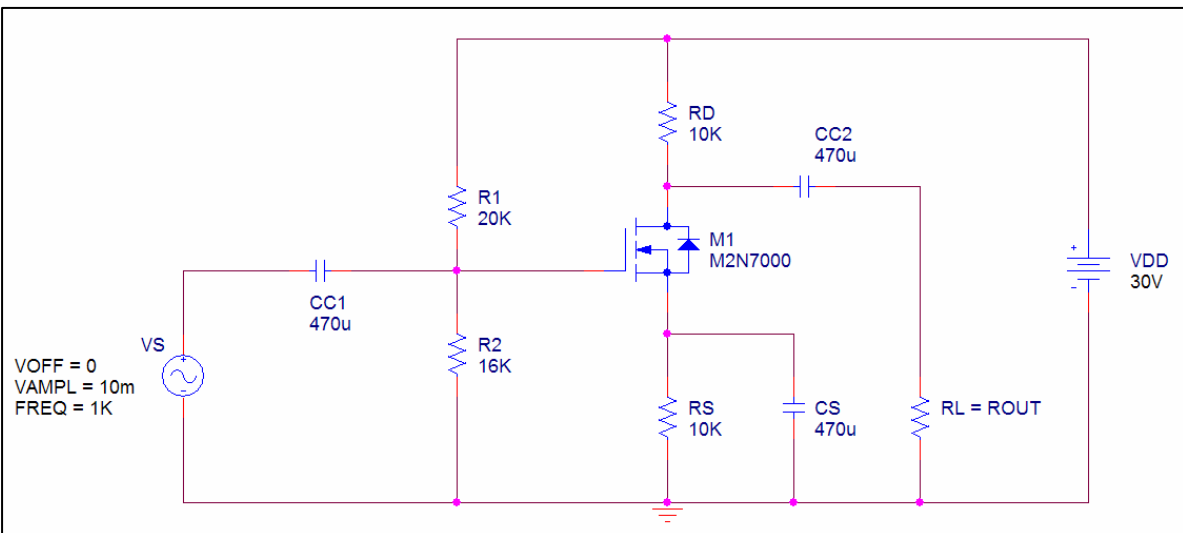

**Figure #2** – MOSFET configured as a CSC (Common Source Configuration) Amplifier

**Figure #3** – (HW) MOSFET configured as a CDC (Common Drain Configuration) Amp

#### **4.- Verification**

Build and fully test the circuits shown in Figure #2 & Figure #3. Applying a sinusoidal signal,  $V_s$  (using the function generator), such that the small signal approximation holds (use  $V_s=10\text{mV}$  at  $1\text{KHz}$ ), measure:

1. Build the CSC Amplifier from Figure #2:
  - a. Voltage gain  $A_{v0}$  the assembled circuit for the *unloaded* case (no  $CC2$  or  $RL$ ). Repeat and find  $A_v$  with a load of  $RL=R_{OUT}$ . Use the oscilloscope to compare  $V_S$  to  $V_{out}$
  - b. Find  $R_{IN}$  (input impedance) and  $R_{OUT}$  (output impedance) of the assembled circuit.
  - c. Find the maximum input voltage that the amplifier can accept before the output distorts (loaded case  $RL = R_{OUT}$ ). Plot the output signal and the corresponding input.
  - d. Determine the phase relationship between the input and output voltages.
  - e. Compare the measured results to your analysis calculations.
  
2. Build the CDC Amplifier from Figure #3. (***note***: This portion may be skipped to save lab time – this is at the discretion of your GTA):
  - a. Voltage gain  $A_{v0}$  the assembled circuit for the *unloaded* case (no  $CC2$  or  $RL$ ). Repeat and find  $A_v$  with a load of  $RL=R_{OUT}$ . Use the oscilloscope to compare  $V_S$  to  $V_{out}$ .
  - b. Find  $R_{IN}$  (input impedance) and  $R_{OUT}$  (output impedance) of the assembled circuit.
  - c. Find the maximum input voltage that the amplifier can accept before the output distorts (loaded case  $RL = R_{OUT}$ ). Plot the output signal and the corresponding input.
  - d. Determine the phase relationship between the input and output voltages.
  - e. Compare the measured results to your analysis calculations.

**Hint:** Connect a large capacitor between  $V_{CC}$  and ground in order to remove all the noise from the source. The noise is amplified and mixes with the output. You may also apply a bandpass filter to channel 1 of the digital oscilloscope to reduce the noise.

## 5.- (HW) Design of Common Source

Design a Common Source voltage amplifier (with shorting capacitor) similar to the one shown in Figure # 1. Use SPICE to verify that all the specifications have been achieved.

### Design Specifications of the Amplifier

- **VDD = 18 V DC**
- **RL = 5 k $\Omega$**
- **|AV| ~ 30 (with RL). |AV| > 30 is even better!**
- **750 k $\Omega$  < RIN < 10 k $\Omega$  — R1 and R2 should be in the k $\Omega$  range**
- **Vin max(before distortion)  $\geq$  60 mVpeak (when loaded with RL=5 k  $\Omega$ )**
- **Maximum Power must occur when loaded with RL= 5 k  $\Omega \pm 5\%$**

(Recall maximum power transfer theorem related to thevenin's theorem)

### *Assumptions:*

- **K = 64 mAmp/Volt<sup>2</sup>**     ***note:* K =  $k_n'$  (W/L)**
  - **Vth = 1.73 V**
  - **Vs = Vds = 1/3(VDD)** ("Rule of Thumb" from textbook)
  - **RD = RS**, and that  $r_0 \gg RD$  and  $r_0 \gg RS$
- 
- Find R1, R2, RD & RS, as well as all voltages/currents. Show all design calculations.
  - Compare the SPICE results to your design calculations and specifications and explain any and all differences.

## **6.- Assembly, Test and Verification of Specifications**

Build and test your design. Measure and verify that your design meets all the given specifications.

- a. Measure  $V_G$ ,  $V_S$ ,  $V_D$ , and  $I_D$  with no input.
- b. Measure  $A_{vo}$ ,  $A_v(R_L= \text{at max power transfer})$ ,  $R_{in}$  (input impedance) and  $R_{out}$  (output impedance) of the assembled circuit.
- c. Find the maximum input voltage that the amplifier can accept before the output distorts.
- d. Measure the phase relationship between the input and output voltages.

## **5.- Conclusion**

- a. Considering that these amplifiers are quite typical, what can you say about  $R_{in}$ ,  $R_{out}$ , and the  $A_v$  for the CSC and CDC amplifiers.
- b. Based on your observation, what are the primary differences between BJT and MOSFET Amplifiers?
- c. Compare the measured results to your design calculations and specifications. Explain any and all differences!