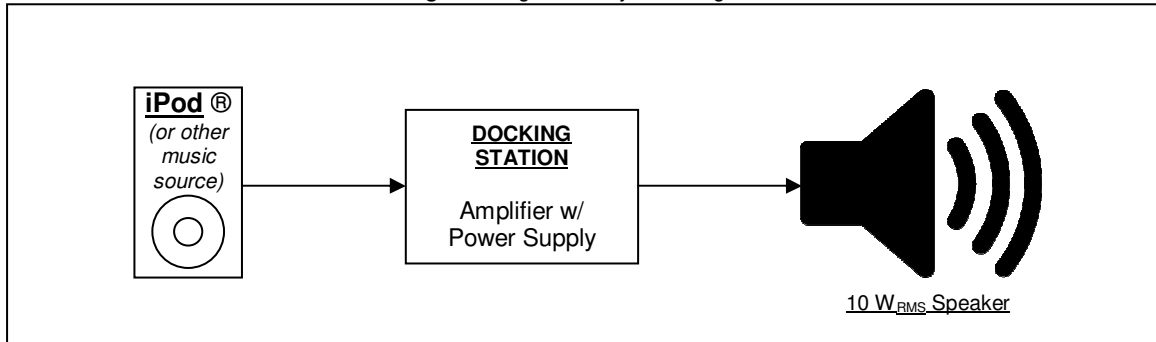


**The George Washington University
School of Engineering and Applied Science
Department of Electrical and Computer Engineering
ECE 20 - Final Project**

Project Description:

You have been hired at Apple Computer Inc. as a summer intern. You have been asked to design an inexpensive iPod® docking station to be sold during the holiday season. Essentially, your task is to design and build a music amplifier, with a power supply, that will meet the specifications below.

Fig 1.1 – High Level System Diagram



Specifications

- Power supply: 120 V_{RMS} at 60 Hz.
- Input Signal (v_{in} , not v_{sig}) = 350mV_{RMS}, *frequency*: entire audio frequency range
- Load: 8Ω speaker
- Output Power: **10 W_{RMS}** +/- 10%
- Volume Control Required
- LED indicator for Power Supply

Requirements

- At minimum, a 2 stage amplifier design must be employed
- A Darlington Configuration for the output stage is suggested to achieve output power requirement

Extra Credit

- FET/BJT Darlington output stage
- Class AB (Push-Pull) output stage
- Class AB (Push-Pull) using Darlington configuration

Due Dates

- 12/4/08 - Initial Project Calculations & simulations
- 12/9/08 (tentative) - Project Demonstration, Oral Presentation, Written Report

Project Demonstration

- Circuit will be tested using function generator set at 350mV_{RMS} at 3 frequencies: 440Hz, 1kHz, 10kHz to verify output power with oscilloscope
- Verification of volume control will be performed
- Amplifier will then be tested using music, grade for clarity of sound will be given.

Oral Presentation

- 10 minute presentation with 5 minute question and answer period. All presentations must be done using MS Power Point.
- Recommended structure of oral report is as follows:
 - System Architecture Overview
 - Discuss the stages of each part of the design
 - Initial Calculations (similar to tutorial #7)
 - Discuss the Rin/Rout for each stage in the design

iPod® is a trademark of Apple, Inc., registered in the U.S. and other countries. All rights reserved.

- Discuss the selection of VCC
- Discuss the selection of transistors (using SPEC sheet data)
- Discuss the initial output voltage and current swing's you've calculated to reach the specified goals
- *You are basically walking viewer through your design process*
- Design of each stage
 - Why did you choose the type of output stage you chose?
 - Hand Calculations (bias voltage/currents, Resistor values, Capacitor values)
 - SPICE simulations showing bias point and transient simulation to verify simulations
- Brief discussion on midterm power supply
 - Treat design as a black-box, you've already covered this in midterm-project no need to explain each step. Just cover the basics (type of rectifier, input output voltage/current, load/ripple)
 - Current/Voltage limitations – using SPEC sheet data
- Implementation
 - Picture of the final circuit
 - Discuss measured Rin/Rout of each stage
 - Discuss measured bias voltages
 - Discuss/Show output voltage swing for each stage
 - Discuss gain for each stage
- Conclusions
 - % error for measured data vs. hand calculated vs. simulated data
 - How did your project compare to your calculations?
 - What would you do differently? How could you improve your design?

Written Report

- A discussion of system architecture (the big-picture), design decisions, Rin/Rout, should be discussed up-front
- Each stage of the project: iPod, CE, CC, speaker, power supply should be given its own sub-section, show hand calculations, SPICE simulations, measured data for each component
- The entire amplifier should then be given a sub-section. Show expected input/output voltage/current swings, SPICE simulations, measured data for entire system
- Discuss the % error between hand/SPICE/measurements in each stages sub-section
- Discuss difficulties encountered, changes you'd make, lessons learned in the conclusion
- All hand calculations must be submitted as an appendix to your report

Grading

- 50% Demonstration
- 25% Oral Report
- 25% Written Report

Extra Credit Criteria

- Extra Credit will be performed if and only if the following criteria have been met:
 - Advanced output stages (class AB, etc.) have successfully been implemented in the final project and are verified during demonstration.
 - Hand calculations, SPICE simulations, and demonstration have been performed.
 - Student can answer any and all questions regarding basic operation, and discuss calculations during oral presentation
- The reward for extra credit will be:
 - Dropping of lowest quiz grade
 - Dropping of two lowest lab report grades
- Students are forewarned from using output stage configurations that they do not fully understand; putting something together and it just “works” is unacceptable and will hurt your final grade.

**The George Washington University
School of Engineering and Applied Science
Department of Electrical and Computer Engineering**

ECE 20 - Final Project Grading Sheet

Student's Name: _____

=== CIRCUIT DEMONSTRATION (100pts total)===

(student must have each item with circuit to show TA during demonstration)

Architecture/Setup

- ____ (5pts) Student is able to discuss architecture (CE – CC, type of output stage etc.)
- ____ (5pts) Student has characterized music source output impedance and speaker impedance
- ____ (5pts) Student is able to explain (calculation/spice) output voltage (V_{peak}) necessary to achieve $10Watt_{RMS}$ goal

Complete Amplifier

- ____ (2.5pts) Student explains value v_{sig} must be to obtain $v_{in} = 350mV_{RMS}$ using function generator *(in context to R_{in} of input stage of amplifier)*
- ____ (2.5pts) Student explains value v_{sig} must be to obtain $v_{in} = 350mV_{RMS}$ using music source *(in context to R_{in} of input stage of amplifier)*

Using VCC: Agilent E3631A DC Power Supply & Vsig = Lab function generator

- ____ (5pts) Scope verifies target V_{peak} across speaker for $v_{in} = 350mV_{RMS}$, 440Hz Tone
- ____ (5pts) Scope verifies target V_{peak} across speaker for $v_{in} = 350mV_{RMS}$, 1KHz Tone
- ____ (5pts) Scope verifies target V_{peak} across speaker for $v_{in} = 350mV_{RMS}$, 10KHz Tone

Using VCC: Agilent E3631A DC Power Supply & Vsig = Music Source – iPod, computer, etc.

- ____ (5pts) Student explains what value v_{sig} must be to obtain $v_{in} = 350mV_{RMS}$ *(in context to R_{in} of input stage of amplifier)*
- ____ (5pts) Scope verifies target V_{peak} across speaker for $v_{in} = 350mV_{RMS}$, all 3 tones
- ____ (5pts) Scope verifies target V_{peak} across speaker for $v_{in} = 350mV_{RMS}$, tone = music
- ____ (5pts) Music Clarity (distortion free, no clipping, etc.)

Using VCC: Midterm Power Supply & Vsig = any source

- ____ (5pts) Scope verifies VCC = 12V/-12V, ripple at minimum
- ____ (5pts) Scope verifies target V_{peak} across speaker for $v_{in} = 350mV_{RMS}$, all 3 tones & music
- ____ (5pts) If ripple too high to produce distortion free music, student explains why

Input Stage

- ____ (5pts) Scope verifies that gain matches student calculation
- ____ (5pts) R_{in}/R_{out} measured/verified
- ____ (5pts) Quiescent Current verified/matches calculations

Output Stage

- ____ (5pts) Scope verifies that gain matches student calculation
- ____ (5pts) R_{in}/R_{out} measured/verified
- ____ (5pts) Quiescent Current verified/matches calculation
- ____ (Y/N) Extra Credit Attempted

=== ORAL PRESENTATION (100 pts total)===

System Architecture Overview

- ____(5pts) Discuss the stages of each part of the design Initial Calculations (similar to tutorial #7)
- ____(5pts) Discuss the R_{in}/R_{out} for each stage in the design
- ____(5pts) Discuss the selection of VCC
- ____(5pts) Discuss the selection of transistors (using SPEC sheet data)
- ____(5pts) Discuss the initial output voltage and current swing's you've calculated to reach the specified goals

Design of each stage

- ____(5pts) Why did you choose the type of output stage you chose?
- ____(5pts) Hand Calculations (bias voltage/currents, Resistor values, Capacitor values)
- ____(5pts) SPICE simulations showing bias point and transient simulation to verify simulations

Brief discussion on midterm power supply

- ____(5pts) Just cover the basics (type of rectifier, input output voltage/current, load/ripple)
- ____(5pts) Current/Voltage limitations – using SPEC sheet data
- ____(5pts) Ripple recalculated for Amplifier as load

Implementation

- ____(2.5pts) Picture of the final circuit
- ____(5pts) Discuss measured R_{in}/R_{out} of each stage
- ____(5pts) Discuss measured bias voltages
- ____(5pts) Discuss/Show output voltage swing for each stage
- ____(5pts) Discuss gain for each stage

Conclusions

- ____(5pts) % error for measured data vs. hand calculated vs. simulated data
- ____(5pts) How did your project compare to your calculations?
- ____(2.5pts) What would you do differently? How could you improve your design?
- ____(10pts) Students Overall Understanding of what he/she has designed and built