

The George Washington University
School of Engineering and Applied Science
Department of Electrical and Computer Engineering
ECE 20 – SPICE Tutorial 3

Parametric Sweep Simulation of a BJT

Description:

In this tutorial we discuss how to generate a typical IV-curve for a Bipolar Junction Transistor (BJT) in SPICE. To do this a DC Sweep simulation will be combined with a parametric simulation.

Background:

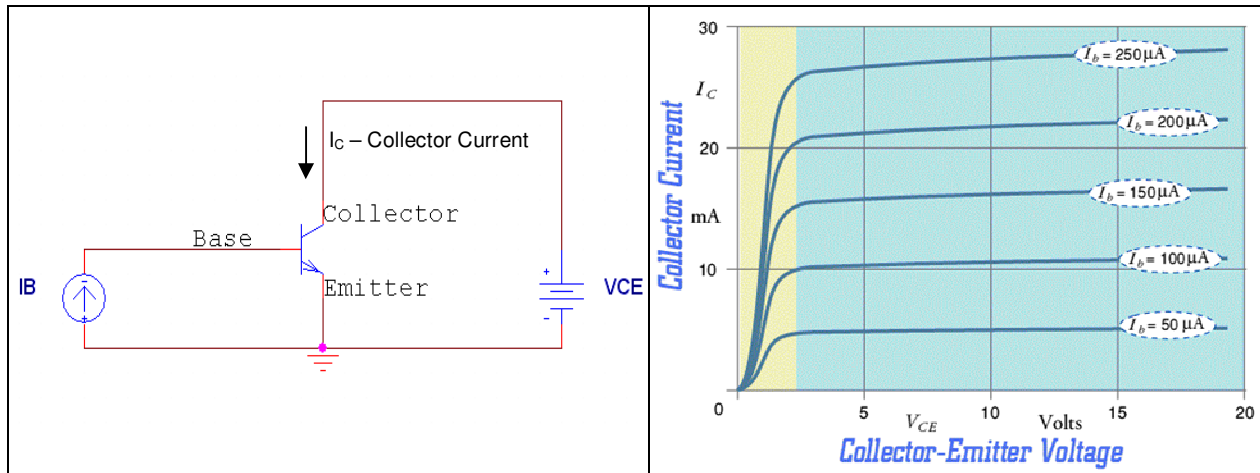


Fig 1: BJT Test Circuit

Fig 2: BJT IV-Curve [1]


A Bipolar Junction Transistor (BJT) is a 3 terminal non-linear device. Current applied to the base of the transistor (I_B) controls the amount of current that will flow from the Collector to the Emitter (I_C). In theory this is a “Current Controlled Current Source” (CCCS). I_B is the “control,” and the Collector-Emitter terminals act like those of a “current source” where the current is I_C .

In order to “turn on” the BJT device, we follow a two step process: 1) Apply voltage across the Collector-Emitter terminals (V_{CE}). 2) Apply current to the base terminal (I_B). Then current (I_C) will flow from the collector to the emitter, behaving as a current source.

Two “characterize” the full range of operation of the device, we vary both V_{CE} and I_B to see the variation in I_C . The test circuit used to characterize a BJT device is shown in Figure 1 above. The typical IV-Curve that this test circuit will produce is shown in figure 2 above. This tutorial will explain how to produce the IV-Curve in figure 2 using SPICE.

Plotting a single IV-Curve for the BJT:

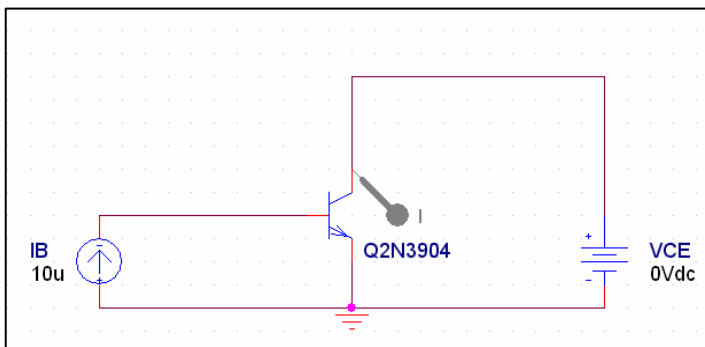
1) Build the following schematic in SPICE:




You will need the following parts:

IDC / SOURCE
VDC / SOURCE
GND (change name to 0)
Q2N3904 / EVAL
A Current Probe

- By default, the current source (IDC) and voltage source (VDC) will be named I1 and V1 respectively, rename them to IB and VCE as you see in the schematic above
 - Make certain that the current source (IB) is upwards, ensuring that current will go 'into' the base of the transistor
 - Set VCE=0V and IB=10uA
- 2) With IB pushing 10uA into the base of the transistor, we will now sweep VCE from 0 to 10V, and observe its effect on I_C
- Create a new simulation profile
 - Set the "Analysis Type" to be a **DC Sweep**
 - Set the "Sweep Variable" to be a Voltage Source, and place the name of the voltage source you wish to sweep in the "Name" fill-in
 - Set the start value for VCE to be 0V and the end value to be 10V
 - Set VCE to be swept in .1V increments

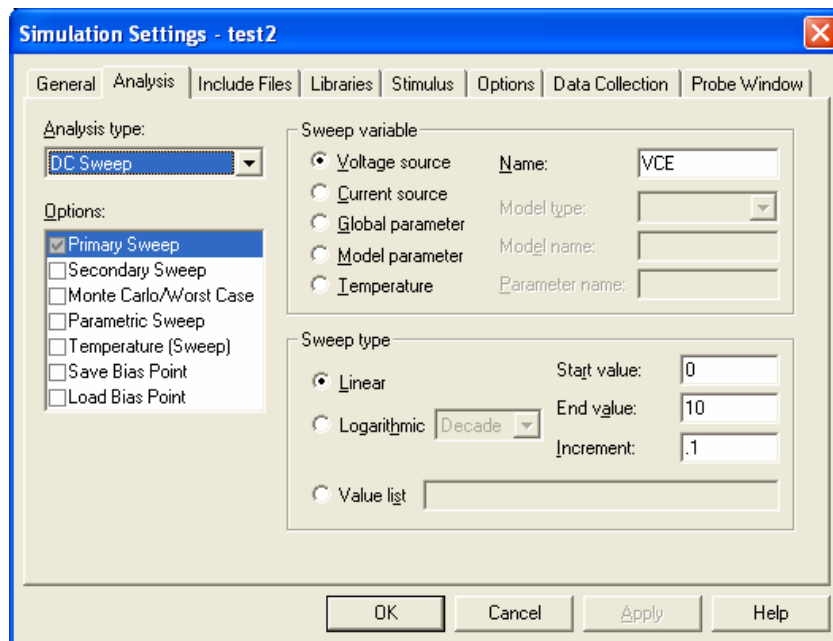

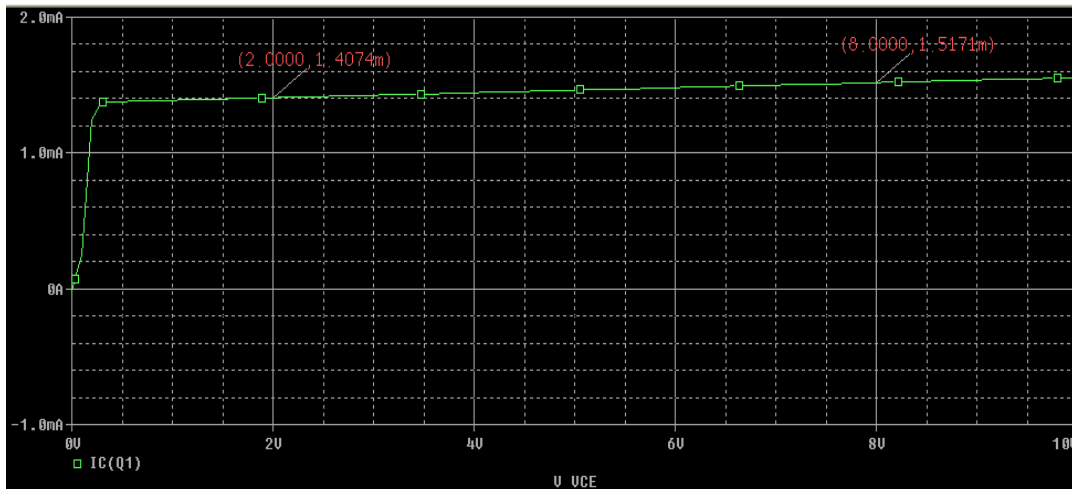3) Run the simulation, the following graph should result:



- This is a single IV-curve for a BJT
- Notice that the X-axis is the 'swept variable' (V_{CE})
- The Y-variable is I_C – the current flowing into the collector of the transistor
- We remember from the schematic that I_B is fixed at 10uA

From the markers on the graph we can interpret the following:


- When $I_B=10\mu A$ and $V_{CE}=2V$, the collector current $I_C=1.407mA$
- When $I_B=10\mu A$ and $V_{CE}=8V$, the collector current $I_C=1.517mA$

We now wish to perform a simulation where I_B is not at a fixed value.

Plotting a family of IV-Curves for the BJT:

In the simulation above, I_B was fixed at $10\mu\text{A}$ while V_{CE} was swept. But we'd like to see how the BJT behaves if both V_{CE} was swept *and* I_B was changed to different values. This is known as a DC-Sweep combined with a Parametric Sweep, often called a "parametric simulation." In our case I_B is the 'parameter' we wish to vary while V_{CE} is swept.

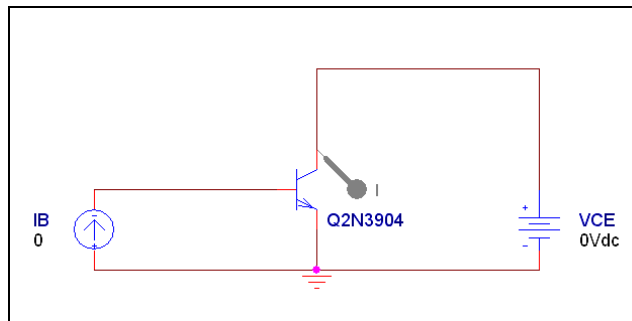
1) Change the schematic built in the first portion of this tutorial to match the following schematic:



- The only difference is that now I_B is set to 0A

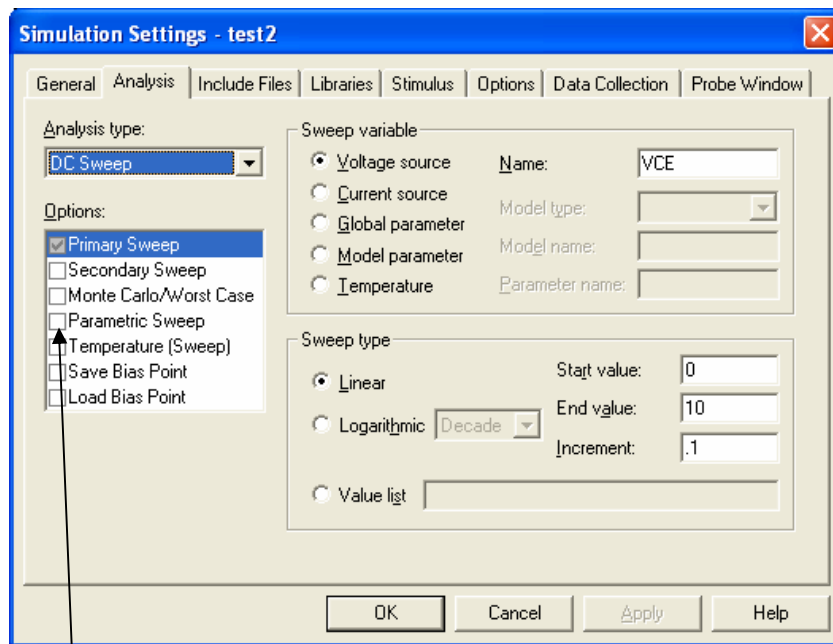
2) Edit the simulation profile from the previous simulation as follows:

- Keep the same settings for the DC-Sweep of V_{CE} :




- Now click on the "Parametric Sweep" check box

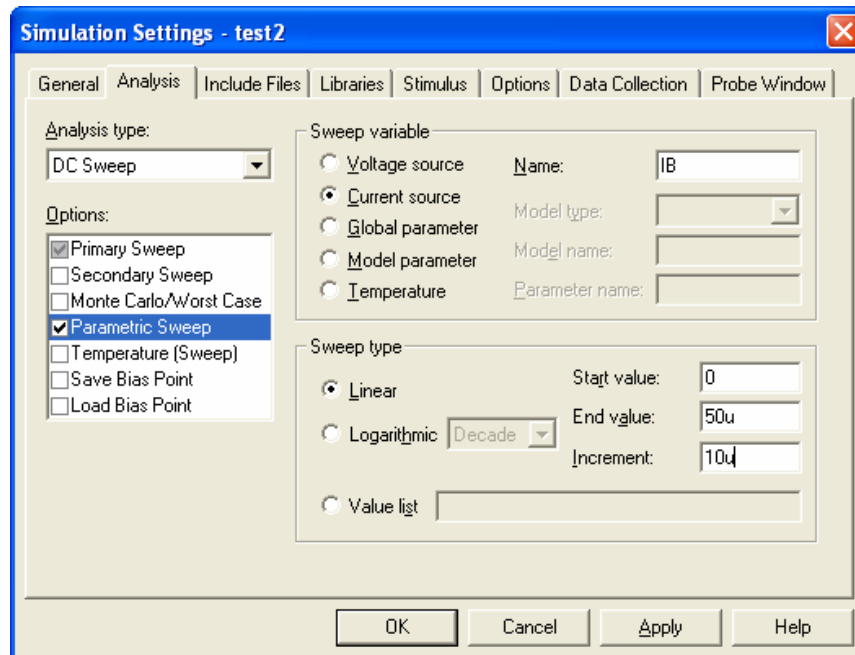- 3) For the Parametric Sweep settings, we want to vary I_B from 0 to 50 μ A in steps of 10 μ A
 - Set the sweep variable to be a 'current source'
 - Set the sweep variable's name to be ' I_B '
 - Set the start value for $I_B=0$ A and the end value to be 50 μ A
 - Set the increment for I_B to be 10 μ A



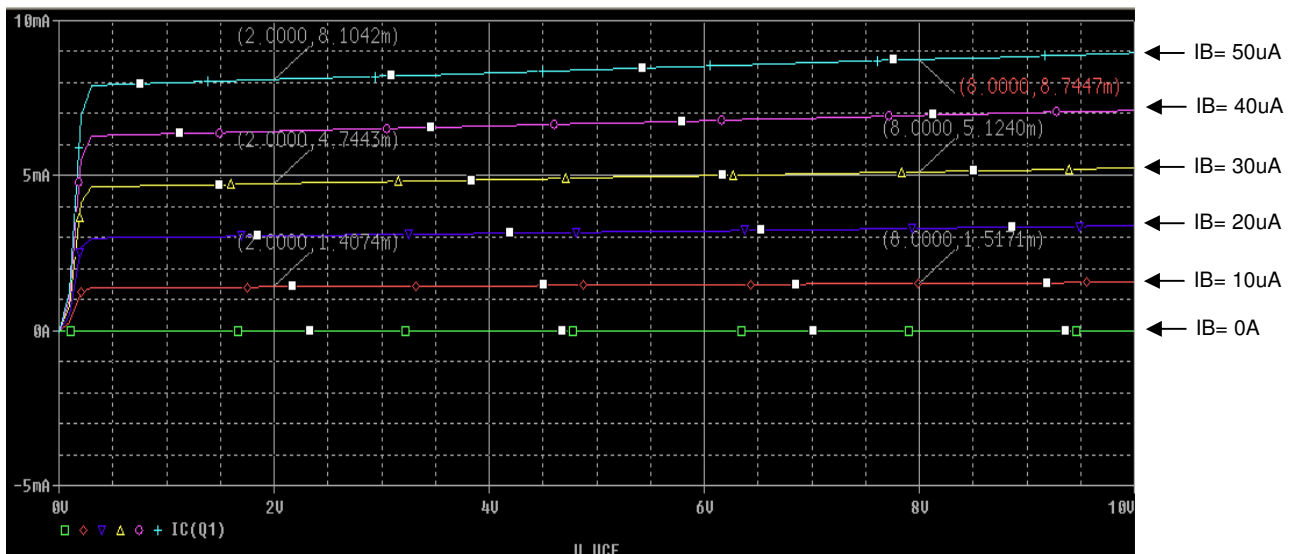- 4) Run the simulation, the following graph will appear:



- This is called a 'family' of IV-Curves for the BJT
- The X-axis is still the DC Swept Variable (V_{CE})
- The Y-variable is still I_C – the current flowing into the collector
- But now there is 1 IV-Curve for each value of I_B that we specified: 0 μ A, 10 μ A, 20 μ A, 30 μ A, 40 μ A, and 50 μ A.

From the markers on the graph (on the RED curve) we can interpret the following:

- When $I_B=10\mu\text{A}$ and $V_{CE}=2\text{V}$, the collector current $I_C=1.407\text{mA}$
- When $I_B=10\mu\text{A}$ and $V_{CE}=8\text{V}$, the collector current $I_C=1.517\text{mA}$

(Notice that this is exactly the same as before!)

From the markers on the graph (on the Top BLUE curve) we can interpret the following:

- When $I_B=50\mu\text{A}$ and $V_{CE}=2\text{V}$, the collector current $I_C=8.1042\text{mA}$
- When $I_B=50\mu\text{A}$ and $V_{CE}=8\text{V}$, the collector current $I_C=8.744\text{mA}$

(Notice that this is exactly the same as before!)

We could use markers on each curve to find the value of I_C at varying values of V_{CE} .

What is incredibly important to take away from the second graph is the effect of I_B on the transistor. Notice that I_C (the collector current) is small ($\sim 1.5\text{mA}$) when I_B is small ($10\mu\text{A}$) for the given values of V_{CE} . But when we increase I_B to $50\mu\text{A}$, I_C is much, much higher ($\sim 8.5\text{mA}$) for the same values of V_{CE} ! In effect I_B has 'controlled' the value of I_C , showing how this device behaves as a "current controlled current source." It can be confusing, but if you look at the graph and ask questions in lab, this will be clearer.

References:

[1] University of Saint Andrews, "Curves Characteristic," The Physics and Astronomy Website, Date Unknown.

<http://www.st-andrews.ac.uk/~www_pa/Scots_Guide/info/comp/active/BiPolar/bpcur.html>