

**The George Washington University  
School of Engineering and Applied Science  
Department of Electrical and Computer Engineering  
ECE 20 – SPICE Tutorial 6**

*Designing a Common-Collector Amplifier*


**Background:**

In the previous lab you design a common-emitter (CE) amplifier. Voltage gain ( $A_v$ ) is easy to achieve with this type of amplifier. As you discovered the input impedance ( $R_{IN}$ ) of the CE is moderate-to-high (on the order of a few kilo-Ohms). The output impedance ( $R_{OUT}$ ) is high (roughly the value of  $R_C$ ). This makes the common-emitter amplifier a poor choice for 'driving' small loads.

A common-collector (CC) amplifier typically has a high input impedance (typically in the hundred kilo-Ohm range) and a very low output impedance (from 1 to ~tens of Ohms). This makes the common-collector amplifier excellent for 'driving' small loads. As you discovered in lab 5, the common-collector amplifier has a voltage gain of about 1, or unity. The common-collector amplifier is considered a voltage-buffer, as the voltage gain is unity, the voltage signal applied at the input will be duplicated at the output; for this reason the common-collector amplifier is typically called a "emitter-follower amplifier." The common-collector amplifier can be thought of as a current amplifier.

When the common-emitter amplifier is cascaded to a common-collector amplifier, the CC can be thought of as an 'impedance transformer.' It can take the high output impedance of the CE amplifier and 'transform it' to a low output impedance capable of driving small loads.

Figure 1.1 shows a typical configuration for a common-collector amplifier. The input voltage is applied to the base while the output voltage is measured at the emitter.

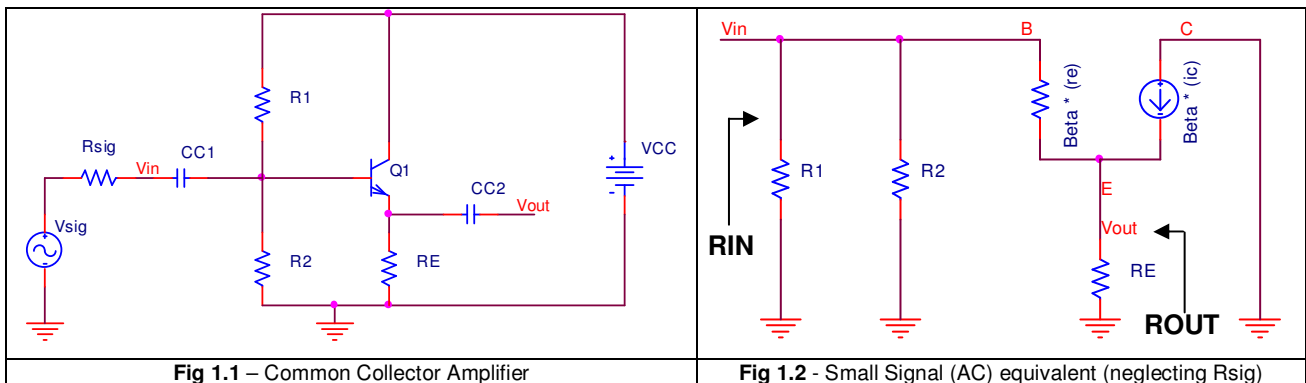

From the AC equivalent of the common-collector amplifier in figure 1.2, we can derive the input impedance, output impedance, and voltage gain:

$$R_{IN} = R1 \parallel R2 \parallel [\beta r_e + (\beta + 1) RE] \quad (\text{no load}) \quad (\text{Remember: } r_e = V_T / I_E, \text{ where } V_T = 26\text{mV})$$

$$R_{OUT} = RE \parallel r_e \quad \text{but } r_e \ll RE \rightarrow Z_o \approx r_e \quad (\text{notice this is VERY small})$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{(\beta + 1) i_b * RE}{(\beta) i_b (r_e) + (\beta + 1) i_b (RE)} \cong \frac{(\beta) i_b * RE}{(\beta) i_b (r_e + RE)} = \frac{RE}{(r_e + RE)}, \quad \text{but since } r_e \ll RE, \text{ then:}$$

$$A_v \approx 1$$

### Designing a Common-Collector Amplifier

Problem: Design a Common-Collector Amplifier using the 2N3904 transistor that meets the following specifications:

$$\begin{aligned} I_C &= 1\text{mA} \\ V_{CC} &= 20\text{ Volts} \\ R_{in} &= 70\text{K}\Omega \\ R_L &= 510\Omega \\ v_{in} &= 10\text{mV @ } 10\text{kHz} \end{aligned}$$

#### Step 1) Determine the size of $R_E$

- We typically make  $V_E = \frac{1}{2} V_{CC}$ , to ensure the largest possible symmetric output voltage swing (around  $V_E$ )
- It is safe to assume that  $I_E \approx I_C$
- Calculate the value of  $R_E$

#### Step 2) Determine the "Q" point of the transistor

- Because you now know  $V_{CE}$  &  $I_C$ , you can use the same procedure from the "Designing a Common-Emitter Amplifier Tutorial" to create an IV-curve for the transistor & determine the Q-point of the transistor. This will help you determine the necessary "base current" needed to achieve the specified  $I_C$ .
- Use the Q-point data to find DC values for:  $I_B$ ,  $V_B$ ,  $I_E$ ,  $\beta$

#### Step 3) Use $V_{CC}$ , $V_B$ , $I_B$ , $I_E$ , and $R_{IN}$ , to find $R_1$ and $R_2$

- Follow the procedure from the "Designing a Common-Emitter Amplifier Tutorial" to generate the same 3 equations for  $V_{BB}$  (**eqn 1**);  $R_B$  (**eqn 2**); and  $I_B$  (**eqn 3**).
- Use the equation derived the first part of *this* tutorial for  $R_{IN}$  as **equation 4**.
- Calculate  $R_1$  and  $R_2$  using the 4 equations

#### Step 4) Check your calculations

- Using the  $R_{IN}$  equation, calculate  $R_{IN}$ . Is it 70k?
- Using the  $R_{OUT}$  equation, calculate  $R_{OUT}$ , is it very small?

#### Step 5) Set values for $CC_1$ & $CC_2$

- The impedance of a capacitor  $Z_c = 1/j2\pi fC$ , make  $CC_1$ ,  $CC_2$  look like a 'short' at 10kHz (the input frequency), and make sure the size you choose for  $CC_1$  and  $CC_2$  matches a capacitor value you have in your ECE 20 kit.

#### Step 6) Determine Current Gain ( $A_i$ ) for the amplifier

- Current gain is defined as:  $A_i = I_{out} / I_{in}$
- Use the equations for  $A_v$ ,  $R_{IN}$ , and  $R_{OUT}$ , ohms law & a little algebra to determine the equation for  $A_i$
- Calculate  $A_i$  for your amplifier, verify current gain using a SPICE transient simulation.

#### Step 7) Verify your calculations using SPICE

- Simulate your amplifier. Check the bias-point analysis to determine if your transistor is at the Q-point you desire.
- Perform a transient simulation to verify the Voltage gain, current gain,  $R_{IN}$  and  $R_{OUT}$ .