


CS 135: Computer Architecture I

Digital Logic Circuits


Instructor: Prof. Bhagi Narahari
 Dept. of Computer Science
 Course URL: www.seas.gwu.edu/~bhagiweb/cs135/



Summary of Number Representation

- Binary representation
 - Why binary
 - Unsigned integers
 - 2's complement
 - ASCII
 - Floating point
 - Hex notation
- Other: Bit Vector, Color
 - Position of bit i indicates set membership of element i
 - Color expressed in RGB values (Red, Green, Blue)
- Arithmetic and Logic operations
 - Addition, multiplication, overflow, sign extension
- Machine dependence
 - Eg: integers represented and stored using big endian or little endian


CS 135



What next: Digital Logic Structures

- Chapter 3 of text [P&P]
- Also read the online links posted on lecture notes webpage
- The hardware building blocks and their operations
- Digital Logic structures
 - Basic device operations: CMOS transistor as switch
 - Combinational Logic circuits
 - Gates (NAND, OR, NOT), Decoder, Multiplexer
 - Adders, multipliers
 - Sequential circuits– concept of memory
 - Finite state machines, memory organization
 - Basic storage elements: latches, flip-flops
 - Memory organization basics


CS 135



Recall: what are Computers meant to do ?


- We will be solving problems that are describable in English (or Greek or French or Hindi or Chinese or ...) and using a box filled with electrons and magnetism to accomplish the task.
 - This is accomplished using a system of well defined (sometimes) transformations that have been developed over the last 50+ years.

CS 135

 

- ### Recall: Why use Binary and How to represent data in a computer?
- At the lowest level, a computer is an electronic machine.
 - > works by controlling the flow of electrons
 - > Electrons flowing on the wire when voltage exists
 - Easy to recognize two conditions:
 1. presence of a voltage – we'll call this state "1"
 2. absence of a voltage – we'll call this state "0"

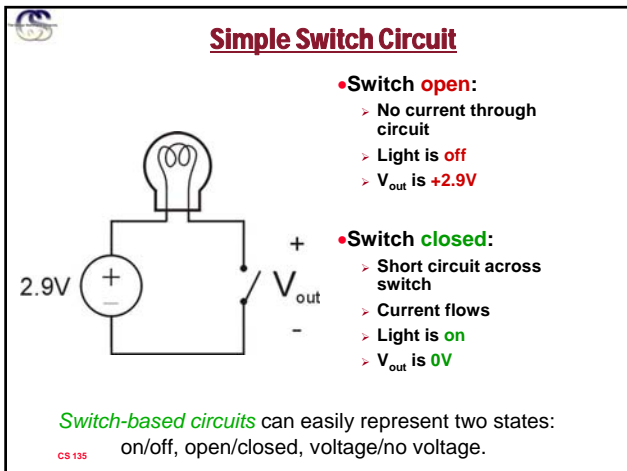More complex to base state on value of voltage
 - Think of the two states 0,1 as states of a switch
 - Changing from 0 to 1 means throwing the switch to turn on the light
 - Presence of voltage on the wire means value of bit = 1 else 0
- CS 135



- ### Digital Circuits: It's all about switching...
- Action at a distance
 - Come here, Watson! I need you!
 - Tubes
 - Transistors
 - CMOS FET
- CS 135

Switching Devices

- **Vacuum Tubes:**
 - Also known as valves because they control the flow of electrons
 - Flow from Cathode to Anode
 - First computer built using vacuum tubes
 - ENIAC
- **Transistors - brought about a big change**
 - Size
 - Speed
 - Precision
- **transistors viewed in digital circuits as a "switch"**
 - Transistors used in analog circuits
 - Stereos, recorders, Image proc., etc.

CS 135

Next Topic...Basics of Digital Circuit Design

- **How to build a switch ?**
 - **Transistors**
- **How to build basic logic functions – gates using transistors ?**
 - **Build simple gates (AND, NOT, OR, ...) using transistors**
- **How to build more complex combinational logic using gates**
 - **Build Adders, multiplexer, decoder, storage devices using simple gates (AND,NOT, OR..)**
- **Build a whole computer using complex logic devices**

CS 135

Transistors

- **An electronic switch that is open or closed between the *source* and the *drain* depending on the voltage on the *gate*.**

CS 135

Transistor: Building Block of Computers

- **Microprocessors contain millions of transistors**
 - Intel Pentium 4 (2000): **48 million**
 - IBM PowerPC 750FX (2002): **38 million**
 - IBM/Apple PowerPC G5 (2003): **58 million**
- **Logically, each transistor acts as a switch**
- **Transistor built using Semiconductor**
- **Combined to implement logic functions**
 - AND, OR, NOT
- **Combined to build higher-level structures**
 - Adder, multiplexer, decoder, register, ...
- **Combined to build processor**
 - LC-3

CS 135

Semiconductor

- **Most materials are either insulators or conductors**
 - They don't "change" their properties
- **Semiconductors: between insulator and conductor**
- **Semiconductors: Based on voltage applied to "gate" it is either insulator or a conductor**
 - Electric field creates a circuit
 - Changes the device from an insulator to a conductor

CS 135

MOS FET (Metal Oxide SemiConductor)

CS 135

CMOS Transistors

- **CMOS**
 - = Complementary Metal-Oxide Semiconductor
 - Standard type for digital applications
 - Two versions: P-type (positive) and N-type (negative)
 - P and N-type transistors operate in inverse modes

P

Open (insulating) if gate is "on" = 1
Closed (conducting) if gate is "off" = 0

N

Open (insulating) if gate is "off" = 0
Closed (conducting) if gate is "on" = 1

CS 135

p-type MOS Transistor

- **p-type**
 - when Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
 - when Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)

Terminal #1 must be connected to +2.9V.

CS 135

n-type MOS Transistor

- n-type complementary to p-type
 - > when Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
 - > when Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)

Terminal #2 must be connected to GND (0V).

CS 135

Computer hardware –what's up

- Let's look back at what we learnt last week
 - > Numbers can be represented as 0s and 1s
 - > 1 is presence of voltage on line, 0 is no voltage on line
 - > Arithmetic operations on these numbers
 - > Logical operations on these numbers
- Starting point: how to implement the basic logic operators using transistors/switches ?
 - > NOT, AND, OR
- Next: how to implement arithmetic operations and other functions
 - > Combinational circuits; example: adder

CS 135

Logical Operations

- NOT, AND, OR, NAND, NOR, XOR
- These are binary functions
 - > Input is binary, output is binary
- Boolean function – operates on boolean variables
 - > Boolean function can be expressed using **truth table**
 - > Eg: addition can be represented as a boolean function
- Recall: can implement a boolean function using AND, OR, NOT, etc.
- Start by building these logical operator “gates” using transistors

CS 135

Logic Gates

- Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.
- Digital symbols:
 - > recall that we assign a range of analog voltages to each digital (logic) symbol

- > assignment of voltage ranges depends on electrical properties of transistors being used
 - > typical values for "1": +5V, +3.3V, +2.9V
 - > from now on we'll use +2.9V

CS 135

Ok...start building logic gates

- Use N type and P type transistors
- 'signal' is a 1 or 0 and nothing else
- Output value will be voltage measured at some point in the "circuit"
 - > Need to determine where to designate the output point (i.e., where to measure)
- Inputs will be applied to the transistor gate
 - > A line in the circuit always tied to 1 (voltage source) and one always tied to 0 (ground)
- Start by looking at the truth table for the logic function

CS 135

NOT Gate

In	Out	In	Out
0 V	2.9 V	0	1
2.9 V	0 V	1	0

CS 135

Inverter (NOT Gate)

In=0 Out=1

In=1 Out=0

Truth table

In	Out	In	Out
0 V	2.9 V	0	1
2.9 V	0 V	1	0





CS 135

NOR Gate

A=0 B=1 C=0

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

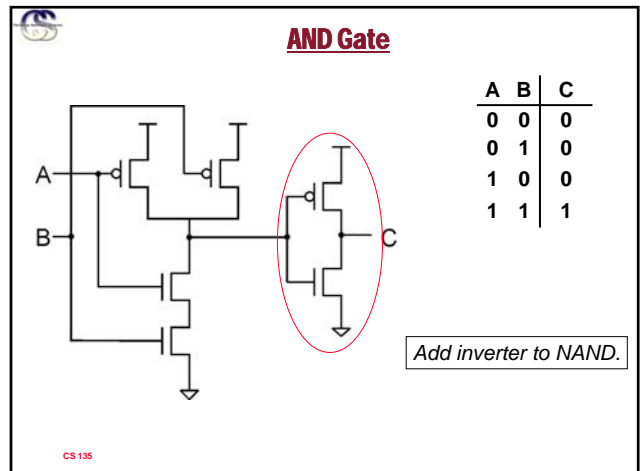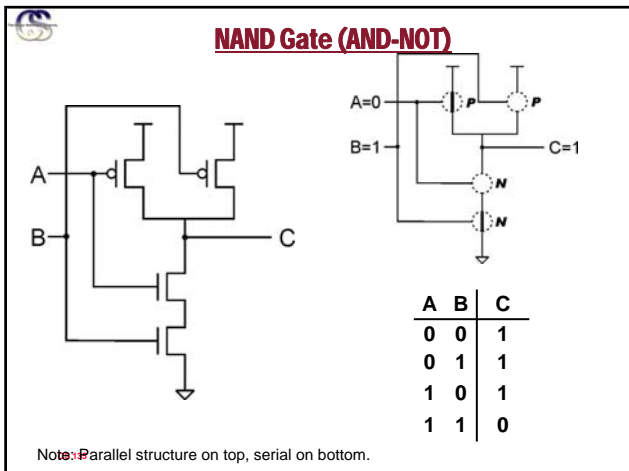  Note: Serial structure on top, parallel on bottom.



Digital Logic Design – Current Summary

- MOS transistors used as switches to implement logic functions.
 - > n-type: connect to GND, turn on (with 1) to pull down to 0
 - > p-type: connect to +2.9V, turn on (with 0) to pull up to 1
- Basic gates: NOT, NOR, NAND
 - > Logic functions are usually expressed with AND, OR, and NOT
- Next: a little theory behind combinational logic design and some basic combinational devices
 - > DeMorgan's Law
 - > Decoder, Multiplexer, Adder, PLA
 - > Boolean Algebra

CS 135

Basic Logic Gates

The diagram shows five basic logic gates with their symbols and Boolean expressions:

- NOT:** A single input A connected to a triangle with a small circle at its tip, resulting in output \bar{A} .
- OR:** Two inputs A and B connected to a curved gate, resulting in output $A+B$.
- NOR:** Two inputs A and B connected to a curved gate with a small circle at its tip, resulting in output $\overline{A+B}$.
- AND:** Two inputs A and B connected to a D-shaped gate, resulting in output AB .
- NAND:** Two inputs A and B connected to a D-shaped gate with a small circle at its tip, resulting in output \overline{AB} .

CS 135

More than 2 Inputs?

- AND/OR can take any number of inputs.
 - > AND = 1 if all inputs are 1.
 - > OR = 1 if any input is 1.
 - > Similar for NAND/NOR.
- Can implement with multiple two-input gates, or with single CMOS circuit.

The diagram illustrates a 3-input AND gate with inputs A , B , and C and output ABC . It shows two ways to implement this:

- Using a single 3-input AND gate symbol.
- Using two 2-input AND gates: the first takes inputs A and B to produce AB , and the second takes AB and C to produce the final output ABC .

CS 135


Digital Logic Circuits

- We saw how we can build the simple logic gates using transistors
- Use these gates as building blocks to build more complex combinational circuits
 - > Decoder: based on value of n-bit input control signal, select one of 2^N outputs
 - > Multiplexer: based on value of N-bit input control signal, select one of 2^N inputs.
 - > Adder: add two binary numbers
 - > ...any boolean function

CS 135

DeMorgan's Law

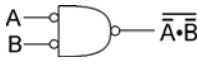- Converting AND to OR (with some help from NOT)
- Consider the following gate:



To convert AND to OR
(or vice versa),
invert inputs and output.

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$	$\overline{A \cdot B}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as A+B

CS 135

DeMorgan's Law

- $\text{NOT}(A \text{ AND } B) = (\text{NOT } A) \text{ OR } (\text{NOT } B)$;
 - > i.e. $\text{NOT}(\text{NOT } A \text{ AND } \text{NOT } B) = A \text{ OR } B$
- $\text{NOT}(A \text{ OR } B) = (\text{NOT } A) \text{ AND } (\text{NOT } B)$;
 - > i.e., $\text{NOT}(\text{NOT } A \text{ OR } \text{NOT } B) = A \text{ AND } B$
- In C syntax:
 - > $\sim(\sim A \& \sim B) = A|B$
 - > $\sim(\sim A|\sim B) = A\&B$

A	B	$\sim A$	$\sim B$	$\sim A \& \sim B$	$\sim(\sim A \& \sim B)$	$\sim A \sim B$	$\sim(\sim A \sim B)$	A B	A&B
0	0	1	1	1	0	1	0	0	0
0	1	1	0	0	1	1	0	1	0
1	0	0	1	0	1	1	0	1	0
1	1	0	0	0	1	0	1	1	1

CS 135

A note on De-Morgan's Law

- Where have you seen this before ?
 - > In a different context ?
- Set operations: Union, Intersect, Comp.
 - > $(A^c \cup B^c) = (A \cap B)^c$
 - > $(A^c \cap B^c) = (A \cup B)^c$
- De-Morgan's law applies to any boolean algebra

CS 135

Completeness: Very Important Concept

- It can be shown that any truth table (i.e. any binary function of binary variables) can be reduced to combinations of the AND & NOT functions, or of the OR & NOT functions.
 - > This result extends also to functions of more than two variables
 - > Methodology: **Karnaugh Maps**
- In fact, it turns out to be convenient to use a basic set of three logic gates:
 - > AND, OR & NOT or NAND, NOR & NOT
 - > In fact, can implement all logic functions using just NAND!

CS 135

Representation of Boolean Logic Functions

- What is this circuit doing ?

CS 135

Boolean Logic Function

- Output(s) is a function of input boolean variables
- $y = f(x, y, \dots)$
- The “operators” used are any of the boolean logic operators
 - > AND, OR, NOT, NAND, etc.
- How do we represent boolean functions?

CS 135

Representation of Logic Functions

- A logic function can be represented as
 - > a truth table
 - > a logic expression
 - > a logic circuit
- Example

$$f = a.(b.c + d) + \bar{a}c = a.b.c + a.d + \bar{a}c$$


a	b	c	d	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

CS 135

Truth tables and Boolean functions

A	B	C	x_1	x_2
0	0	0	0	1
0	0	1	0	0
0	1	0	1	0
0	1	1	1	1
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0


CS 135



Truth Table to Digital Circuit design...

- Look at all rows with a 1 in the output
 - ALL conditions in the input must hold for the output to be 1 = AND of all the input conditions
 - Any row can be 1 = do an OR of all the row conditions
- When is $x_1 = 1$?
 - Look at all rows where $x_1 = 1$
 - What are the values of inputs for each of these rows ?


CS 135



Canonical Boolean expressions with Minterms

- Each row in a truth table specifies values of all the input variables
 - What is the value of each input variable – 0 or 1
 - i.e., $y=1$ or $y'=1$ for each input variable y
- For the specific output, what row(s) are we interested ?
- When is the value of the output =1
 - When the value in the row of the truth table =1
 - What are the values of the input variables ?
- **Canonical boolean expression**
 - Any boolean expression can be converted to an equivalent two level AND-OR expression
 - an OR of AND terms,
 - each AND term corresponds to a 1 in the truth table row,
 - each AND term contains all input variables exactly once – i.e., a minterm
 - **Canonical expression: OR of minterms**


CS 135



Boolean function from a Truth Table

- OR of minterms
- Each minterm is an AND of the input variables y
 - y or y' is true in each row

CS 135



Circuits and Boolean Functions

- How to get boolean function represented by a circuit ?
- Trace each output line through the gates

CS 135



Combinational and Sequential Circuits

- A circuit is a collection of devices that are physically connected by wires
 - Combinational circuit
 - Sequential circuit
- In Combinational circuit the input determines output
- In sequential circuit, the input and the previous 'state' (previous values) determine output and next 'state'
 - Need circuit to implement concept of storage

CS 135



Combinational Devices

- Use basic gates to build more complex combinational logic functions

CS 135



Problem

- You have an n bit binary number assigned as unique ID to each student. How do we select & physically connect to a specific student with ID y ?
- Example:
 - 00 is Sam, 01 is Krista, 10 is Zach, 11 is Alex
 - We want to select Zach:
 - Give binary 10 as input, and the output line to Zach is set to high - 110 volts ☺

CS 135



Boolean function for "selector"

- Need to select one of four:
 - 2 bits needed to encode the four outcomes
 - $a_1 a_0$
- 4 outputs – 1 associated with each signal
 - $x_3 x_2 x_1 x_0$
- What is the boolean function ?
- When is each x_i set to 1:
 - $x_0 = a_1' \cdot a_0'$ (NOT a_1 AND NOT a_0)
 - $x_1 = a_1' \cdot a_0$
 - $x_2 = a_1 \cdot a_0'$
 - $x_3 = a_1 \cdot a_0$

CS 135


Truth table

a_1	a_0	x_0	x_1	x_2	x_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

CS 135

- Truth Table to Digital Circuit design...**
- Look at all rows with a 1 in the output
 - ALL conditions in the input must hold for the output to be 1 = AND of all the input conditions
 - Any row can be 1 = do an OR of all the row conditions
 - When is $x_2 = 1$?
- CS 135

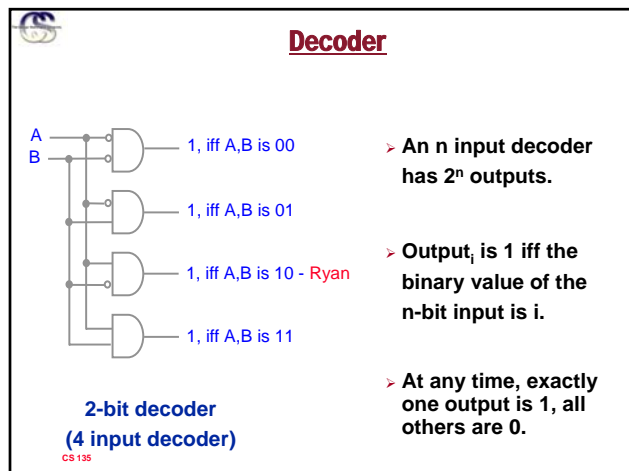- Notation shortcuts...**
- What happens when circle is put at input of AND gate ?
 - Invert signal – same as adding a NOT gate in the input line and then sending it to input of AND gate
- CS 135




Truth Table to Digital Circuit design...

- Look at all rows with a 1 in the output
 - ALL conditions in the input must hold for the output to be 1 = AND of all the input conditions
 - Any row can be 1 = do an OR of all the row conditions

CS 135


Problem: Selecting one of many

- You have m input signals and you want to use the logical value on one of them determined by a set control signals/wires – n control signals
 - Each student sends a signal (0 or 1)
 - I want to select Zach's signal – so I can give him an A grade...
 - Need to give Zach's code of 10 to select his answer

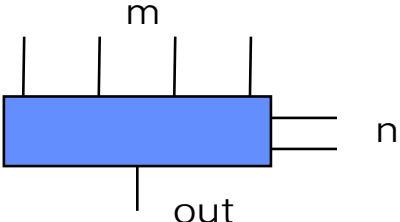

CS 135


Multiplexer (MUX)

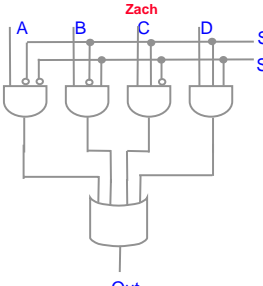

In general, a MUX has

- 2^n data inputs
- n select (or control) lines
- and 1 output.

It behaves like a channel selector.
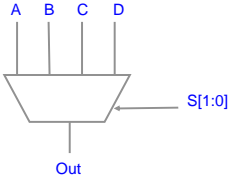
$$\text{Out} = A \cdot \bar{S}_0 \cdot \bar{S}_1 + B \cdot \bar{S}_0 \cdot S_1 + C \cdot S_0 \cdot \bar{S}_1 + D \cdot S_0 \cdot S_1$$


A 4-to-1 MUX:
Out takes the value of A, B, C or D depending on the value of S (00, 01, 10, 11)

CS 135

Problem

- No one will buy your new computer design unless it can do at least some math, say, like adding!
- How to build hardware for adding 2 binary numbers using what we have learnt so far ?
- First look at the function performed by addition – we saw this last week
 - Bit by bit addition, right to left, propagate carry
 - Inputs: A, B and Carry-in
 - Output: sum bit and carry-out (to next bit position)

CS 135

Truth table for Addition


A	B	Carry In	Out	Carry Out
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

CS 135

Truth

A	B	Carry In	Out	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

CS 135

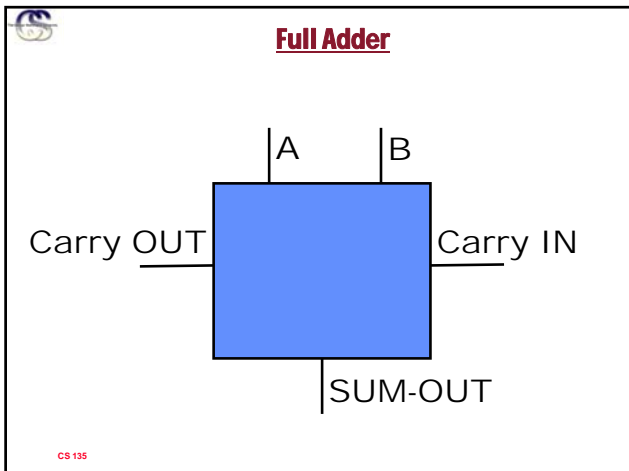

- Boolean function for Addition**
- When is Sum = 1, as a function of A, B, C_{in}
 - > Write function for S
 - $S = A'B'C_{in} + A'BC'_{in} + AB'C_{in}' + ABC_{in}$
 - When is $C_{out} = 1$, as a function of A, B, C_{in}
 - > Write function for C_{out}
 - $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- CS 135

Full Adder

- Add two bits and carry-in, produce one-bit sum and carry-out.

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

CS 135

N-bit Adder

- Use the building block of the full-adder to build N-bit adder
 - Need to connect carry-out to carry-in of next significant bit

CS 135

Four-bit Adder

CS 135

Is there a theory behind design of combinational logic devices ?

- To describe behavior of combinational circuit
 - Truth table
 - Boolean expressions
 - Digital logic circuit/diagram
- Equivalent circuits ?
- Efficient design ?
 - Fewest gates used
- Boolean Algebra: algebraic expression written according to laws of boolean algebra specifies not only what a combinational circuit does, but also how it does it!

CS 135