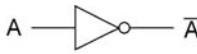


CS 135: Computer Architecture I

Boolean Algebra


Instructor: Prof. Bhagi Narahari
Dept. of Computer Science
Course URL: www.seas.gwu.edu/~bhagiweb/cs135/

Basic Logic Gates




 $A \rightarrow \bar{A}$


NOT


 $A+B$


OR


 $\overline{A+B}$

NOR


 AB

AND


 \overline{AB}

NAND

CS 135

Digital Logic Circuits


- We saw how we can build the simple logic gates using transistors
 - N-type: send 1 to gate to close 'switch'
 - P-type: send 0 to gate to close 'switch'
- Use these gates as building blocks to build more complex combinational circuits
 - Decoder: based on value of n-bit input control signal, select one of 2^N outputs
 - Multiplexer: based on value of N-bit input control signal, select one of 2^N inputs.
 - Adder: add two binary numbers
 - ...any boolean function

CS 135

Theory of Combinational Logic Design ?

- Is there a well grounded theory behind design of boolean logic circuits/functions ?
- Equivalent circuits ?
- Efficient design ?
 - Fewest gates used


CS 135



Boolean Algebra

- To describe behavior of combinational circuit
 - Truth table
 - Boolean algebraic expressions
 - Digital logic circuit/diagram
- Algebraic expression written according to laws of boolean algebra specifies not only what a combinational circuit does, but also how it does it!


CS 135



Truth Table to Digital Circuit design...

- Look at all rows with a 1 in the output
 - ALL conditions in the input must hold for the output to be 1 = AND of all the input conditions
 - Any row can be 1 = do an OR of all the row conditions
- When is $x_1 = 1$?
 - Look at all rows where $x_1 = 1$
 - What are the values of inputs for each of these rows ?


CS 135



Canonical Boolean expressions with Minterms

- Each row in a truth table specifies values of all the input variables
 - What is the value of each input variable – 0 or 1
 - i.e., $y=1$ or $y'=1$ for each input variable y
- For the specific output, what row(s) are we interested ?
- When is the value of the output =1
 - When the value in the row of the truth table =1
 - What are the values of the input variables ?
- **Canonical boolean expression**
 - Any boolean expression can be converted to an equivalent two level AND-OR expression
 - an OR of AND terms,
 - each AND term corresponds to a 1 in the truth table row,
 - each AND term contains all input variables exactly once – i.e., a *minterm*
 - **Canonical expression: OR of minterms**


CS 135



Boolean Algebra – Definitions..recall from CS123

- Boolean algebra has three operations defined over boolean variables:
 - OR (+), AND (.) and complement (')
- Recall fundamental properties of Boolean algebra
 - These apply to anything that is a boolean algebra
 - Sets, digital logic circuits, ...


CS 135



Boolean Algebra– Fundamental Properties

- **Commutative:**
 - $x+y = y+x$ $x.y = y.x$
- **Associative**
 - $(x+y)+z = x+(y+z)$ $(x.y).z = x.(y.z)$
- **Distributive**
 - $x+(y.z) = (x+y).(x+z)$ $x.(y+z)=(x.y)+(x.z)$
- **Identity**
 - $x+0 = x$ $x.1 = x$
- **Complement**
 - $x + (x') = 1$ $x.(x') = 0$


CS 135



Laws of Boolean algebra

- **Duality property:** each boolean property has a dual property
 - Exchange + and . Exchange 1 and 0
- **Many useful properties/theorems can be proved from the 10 fundamental properties**


CS 135



Example: Idempotent Property

- **Prove:** $x + x = x$
- **Proof:** use only the 10 fundamental laws
- $x+x = (x+x).1$; From identity property
- $(x+x).1 = (x+x).(x+x')$; complement
- $(x+x).(x+x') = (x.x) + (x.x')$; distributive
- $x + (x.x') = x + 0$; complement
- $x+0 = x$; identity property
 - QED
- **The duality property is:** $x.x = x$


CS 135



Some useful properties...

- **Zero theorem**
 - $x+1 = 1$ $x.0 = 0$
- **Absorption property**
 - $x + x.y = x$ $x.(x+y) = x$
- **De Morgan's law**
 - $(a.b)' = a' + b'$ $(a+b)' = a' . b'$
 - $(a.b.c)' = a'+b'+c'$ $(a+b+c)' = a'.b'.c'$
- **Complement**
 - $(x')' = x$
 -


CS 135



Two Level Circuits

- Every boolean expression can be transformed to an AND-OR expression
 - Resulting in a 2 level circuit
- Advantage of 2 level circuit ?
 - Gate delays
 - Go through only two levels/layers of gates


CS 135



Why this discussion of Boolean Algebra...

- Every boolean expression has a corresponding logic circuit diagram; and every logic circuit diagram has a corresponding boolean expression
 - One to one correspondence
- But a given truth table can have several corresponding implementations
- How to map from truth table to boolean expression ?
 - How to pick the “best” boolean expression ?


CS 135



Simplification of boolean expressions

- The boolean expression/function
 $x(a,b,c,d) = a'bd' + a'c'd' + a'bc'd'$
- Can be simplified using absorption property to
 $a'bd' + (a'c'd') + (a'c'd')b = a'bd' + a'c'd'$

CS 135



Combinational Circuit Design: Truth Tables and Boolean expressions

- Given truth table we want to find an “efficient” implementation (i.e., circuit)
 - Efficient in speed
 - Efficient in number of gates
 - Simplicity of design
- Canonical boolean expression
 - Any boolean expression can be converted to an equivalent two level AND-OR expression
 - an OR of AND terms,
 - each AND term corresponds to a 1 in the truth table row,
 - each AND term contains all input variables exactly once – i.e., a *minterm*
 - Canonical expression: OR of minterms
- Graphical method for designing two level circuits with 3 or 4 variables using minimum possible number of gates
 - What is this method ????

CS 135

Canonical Expressions

- Consider boolean expression x , where $x(a,b,c) = abc + a'bc + ab$
 - First two are minterms since they contain all three input variables
- $abc + a'bc + ab = abc + a'bc + ab(c+c')$

$$= abc + a'bc + abc + abc'$$

$$= abc + a'bc + abc'$$

Truth table?

CS 135

Example

a	b	c	x
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

CS 135

Transformation of the Boolean expression

- $abc + a'bc + abc'$

$$= (a + a')bc + abc'$$

$$= bc + abc'$$
- $a'bc + abc + abc'$

$$= a'bc + ab(c + c')$$

$$= a'bc + ab$$
- $a'bc + abc + abc'$

$$= a'bc + abc + abc + abc'$$

$$= (a' + a)bc + ab(c + c')$$

$$= bc + ab$$

CS 135

Truth table in 2-dimensions

		bc			
		00	01	11	10
a	0	0	0	1	0
	1	0	0	1	1

← b (b=1) →

↕ (a=a=1)

← c (c=1) →

$x_1 = bc$ $x_2 = ab$

Therefore, $x = a'bc + abc + abc' = bc + ab$

CS 135



Distance between minterms

- Concept of “distance” between two minterms (Hamming distance):
 - Number of variables that are different
 - Distance(abc, abc')=1 only c and c' different
 - Distance($abc, a'bc'$)=2 both a and c are different
- Arrange 2-d truth table so that values in consecutive columns(rows) differ in one bit position

CS 135



Karnaugh Maps

- Graphical way to represent boolean functions
 - Based on concept of distance
- Recognizing adjacent minterms is key to minimization of AND-OR expression
- K-map is a tool to minimize a two level circuit that it makes it easy to spot adjacent minterms
- Karnaugh Map is a truth table arranged so that adjacent entries represent minterms that differ by one.

CS 135



Grouping minterms in K-Map

- Group ‘cells’ in K-map that are adjacent and have a value of 1 in the cell
 - Group of 2 cells in 3 variable K-map: is an AND of two variables
 - Group of 4 cells in 3 variable K-map: is single variable





CS 135




Minimization using K-Maps

- Minimization procedure : determine best set of groups that will cover all the 1's in the K-map
 - “best” means the set that corresponds to a two-level circuit with the least number of gates and the least number of inputs per gate.
 - The number of groups equals number of AND gates
 - We want the smallest number of groups with each group as large as possible such that the groups cover all the 1's


CS 135

 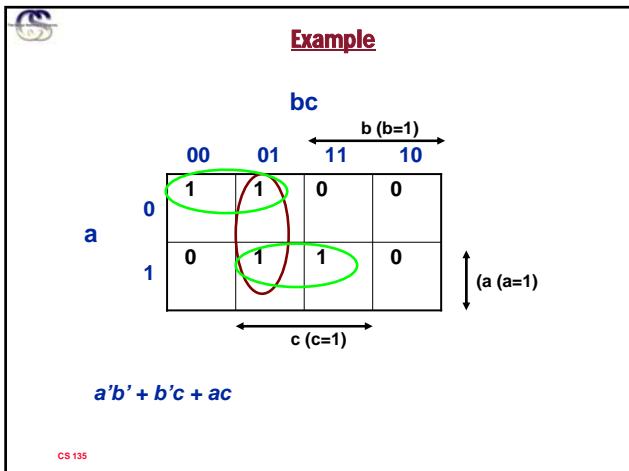  

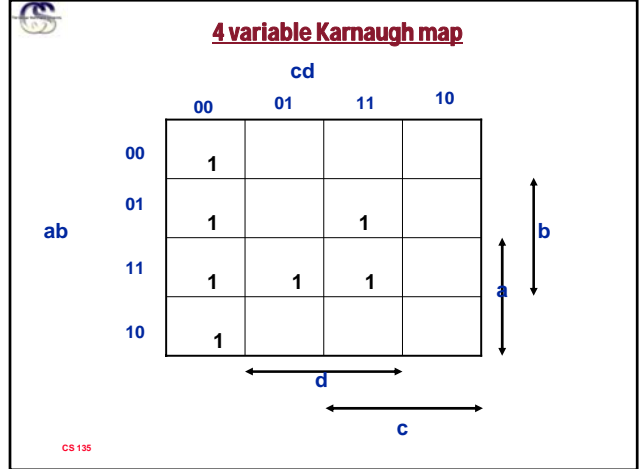

- Summary of Combinational Logic**
- **Combinational device/circuit:** any circuit built using the basic gates
 - **Expressed as**
 - Truth table
 - Digital circuit
 - Boolean function
 - Any boolean function can be expressed as two level function
 - **Minimization procedure: Karnaugh Map**
 - Try to minimize the number of gates, and inputs to gates, in a two level circuit


- Combinational vs. Sequential**
- **Combinational Circuit**
 - always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs
 - **Sequential Circuit**
 - stores information
 - output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
 - *example: vending machine*
 - Current total increases when you insert coins
 - output depends on previous state
 - useful for building “memory” elements and “state machines”



Vending Machine

- **Problem: Read input coins, Keep track of current total.**
 - If total equal to (or greater than) 75 cents then process request
- **What do we need to keep track of ?**
 - Current total (of coins fed into the machine)
 - What is a “state” of the machine
 - Current total!
 - Assume only 5c, 10c, 25cent coins
- **‘transition’ between states ?**
 - Current state 10 goes to
 - next state 15 if input = 5c
 - Next state 20 if input =10c
 - Next state 35 if input=25c

CS 135




Next ... Sequential Logic

- **Build a device, using combinational logic devices, to store a value**
 - RS Latch (also called SR Latch)
- **Implement concept of memory**
- **Methodology behind design of sequential logic circuits**
 - Finite State Machines

- **Combine sequential and combinational logic devices to “assemble” a simple processor!**

CS 135



Sequential Circuits

- **Combinational logic circuits are perfect for situations when we require the immediate application of a Boolean function to a set of inputs.**
- **There are other times, however, when we need a circuit to change its value with consideration to its current state as well as its inputs.**
 - These circuits have to “remember” their current state.
- **Sequential logic circuits provide this functionality for us.**

CS 135