

The George Washington University

Csci 136 Computer Architecture II

–Single-Cycle Datapath

Xuzhen Cheng
cheng@gwu.edu

The George Washington University

Announcements

- **Homework Assignment #7 is due on March 10, before class.**
 - Readings: Sections 5.1-5.4
 - Problems: 5.1, 5.2, 5.8-5.10, 5.13, 5.28.
- **Project #2 is due on 11:59PM, March 10.**
- **Quiz #3: March 29, 2005**

The George Washington University

The Big Picture

- **The Five Classic Components of a Computer**

Processor
Control
Datapath

Memory

Input
Output

- **Performance of a machine is determined by:**
 - Instruction count; Clock cycle time; Clock cycles per instruction
- **Processor design (datapath and control) will determine:**
 - Clock cycle time; Clock cycles per instruction
 - Who will determine Instruction Count?
 - Compiler, ISA

The George Washington University

How to Design a Processor: Step by Step

1. **Analyze instruction set => datapath requirements**
 1. the meaning of each instruction is given by the *register transfers*
 2. datapath must include storage element for registers
 3. datapath must support each register transfer
2. **Select the set of datapath components and establish clocking methodology**
3. **Assemble the datapath meeting the requirements**
4. **Analyze the implementation of each instruction to determine the settings of the control points that effects the register transfer**
5. **Assemble the control logic**

The George Washington University

MIPS Instruction Format

- **All MIPS instructions are 32 bits long. 3 formats:**

- R-type

	31	26	21	16	11	6	0
	op	rs	rt	rd	shamt	funct	
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	

- I-type

	31	26	21	16			
	op	rs	rt	immediate			
	6 bits	5 bits	5 bits	16 bits			

- J-type

	31	26					
	op	target address					
	6 bits	26 bits					

- **The different fields are:**
 - **op**: operation ("opcode") of the instruction
 - **rs, rt, rd**: the source and destination register specifiers
 - **shamt**: shift amount
 - **funct**: selects the variant of the operation in the "op" field
 - **address / immediate**: address offset or immediate value
 - **target address**: target address of jump instruction

The George Washington University

MIPS Instruction Subset for Today

- **ADD and SUB**
 - addu rd, rs, rt
 - subu rd, rs, rt
- **OR Immediate:**
 - ori rt, rs, imm16
- **LOAD and STORE Word**
 - lw rt, rs, imm16
 - sw rt, rs, imm16
- **BRANCH:**
 - beq rs, rt, imm16

inst	Register Transfers
ADDU	R[rd] ← R[rs] + R[rt]; PC ← PC + 4
SUBU	R[rd] ← R[rs] - R[rt]; PC ← PC + 4
ORi	R[rt] ← R[rs] zero_ext(Imm16); PC ← PC + 4
LOAD	R[rt] ← MEM[R[rs] + sign_ext(Imm16)]; PC ← PC + 4
STORE	MEM[R[rs] + sign_ext(Imm16)] ← R[rt]; PC ← PC + 4
BEQ	if (R[rs] == R[rt]) then PC ← PC + 4 + ([sign_ext(Imm16)] << 2) else PC ← PC + 4



Step 1: Requirements of the Instruction Set

- ◆ **Memory**
 - instruction & data: instruction=MEM[PC]
- ◆ **Registers (32 x 32)**
 - read RS; read RT; Write RT or RD
- ◆ **PC, what is the new PC?**
- ◆ **Extender: sign-extension or 0-extension?**
- ◆ **Add and Sub register or extended immediate**
- ◆ **Add 4 or extended immediate to PC**




Step 2: Components of the Datapath

- ◆ **Combinational Elements**
- ◆ **Storage Elements**
 - Clocking methodology



 Combinational Logic Elements (Basic Building Blocks)




Basic Hardware Review

- ◆ **D Latch**
- ◆ **D Flip Flop**




Storage Element: Register (Basic Building Block)

 - ◆ **Similar to the D Flip Flop except**
 - N-bit input and output
 - Write Enable input
- ◆ **Write Enable:**
 - negated (0): Data Out will not change
 - asserted (1): Data Out will become Data In



Storage Element: Register File

- ◆ **Register File consists of 32 registers:**
 - Two 32-bit output busses: busA and busB
 - One 32-bit input bus: busW
- ◆ **Register is selected by:**
 - RA (number) selects the register to put on busA (data)
 - RB (number) selects the register to put on busB (data)
 - RW (number) selects the register to be written via busW (data) when Write Enable is high
- ◆ **Clock input (CLK)**
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as combinational logic:
 - RA or RB valid => busA or busB outputs valid after "access time."

 

Storage Element: Idealized Memory

- Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is selected by:
 - Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory word to be written via the Data In bus
- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid => Data Out valid after "access time."

Clocking Methodology

- All storage elements are clocked by the same clock edge
- Clock Cycle Time must be \geq CLK-to-Q + Longest Delay Path + Setup Time + Clock Skew
- Hold Time is also effected by clock skew
- Need enough time for signal to propagate through

Step 3: Assemble DataPath meeting our requirements

- Instruction Fetch
 - Instruction = MEM[PC]
 - Update PC
- Read Operands and Execute Operation
 - Read one or two registers
 - Execute operation

Datapath for Instruction Fetch







- Fetch the Instruction: mem[PC]
- Update the program counter:
 - Sequential Code: PC \leftarrow PC + 4
 - Branch and Jump: PC \leftarrow "something else"

Datapath for R-Type Instructions

- $R[rd] \leftarrow R[rs] \text{ op } R[rt]$ Example: addU rd, rs, rt
 - Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
 - ALUctr and RegWr: control logic after decoding the instruction

Logic Operations with Immediate

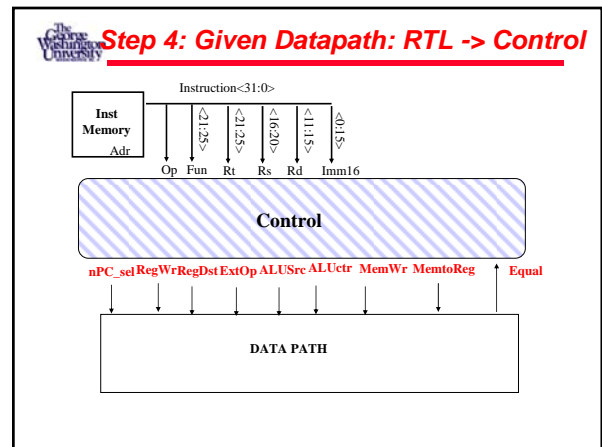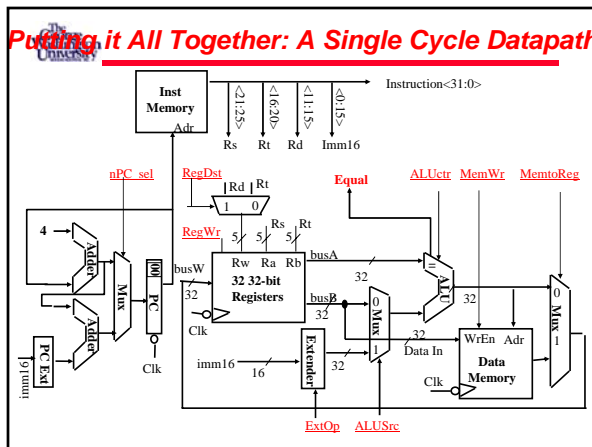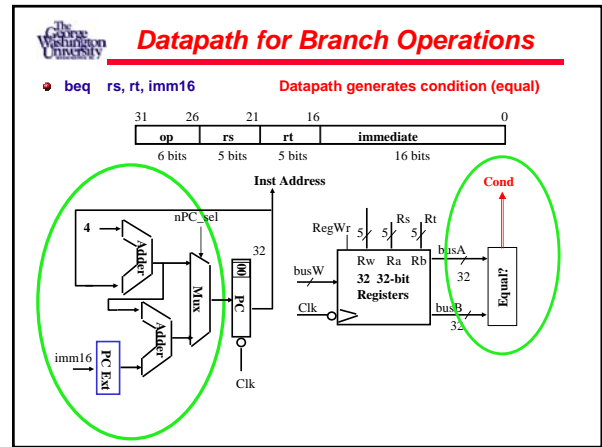 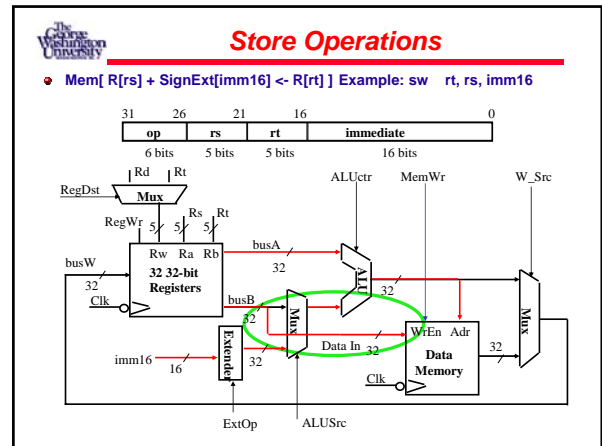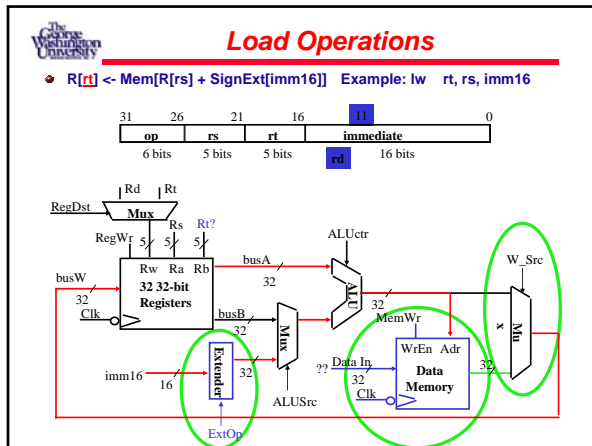$R[rd] \leftarrow R[rs] \text{ op } \text{ZeroExt}[\text{imm16}]$
Eg. Ori \$7, \$8, 0x20



Meaning of the Control Signals

- Rs, Rt, Rd and Imed16 hardwired into datapath
- nPC_sel: 0 => PC <- PC + 4; 1 => PC <- PC + 4 + SignExt(Im16) || 00

Meaning of the Control Signals



- ExtOp: "zero", "sign"
- ALUSrc: 0 => regB; 1 => immed
- ALUctr: "add", "sub", "or"
- MemWr: write memory
- MemtoReg: 1 => Mem
- RegDst: 0 => "rt"; 1 => "rd"
- RegWr: write dest register

Review on ALU Design

ALU Control Lines	Function
0000	And
0001	Or
0010	Add
0110	Subtraction
0111	Slt, beq
1100	NOR

ALU Control and the Central Control

- Two-level design to ease the job
 - ALU Control generates the 4 control lines for ALU operation
 - Func code field is only effective for R-type instructions, whose Opcode field contains 0s.
 - The operation of I-type and J-type instructions is determined only by the 6 bit Opcode field.
 - Lw/sw and beq need ALU even though they are I-type instructions.
 - Three cases: address computation for lw/sw, comparison for beq, and R-Type; needs two control lines from the main control unit: ALUOp: 00 for lw/sw, 01 for beq, 10 for R-type
- Design ALU control
 - Input: the 6 bit func code field for R-type
 - Input: the 2 bit ALUOp from the main control unit.
- Design the main control unit
 - Input: the 6 bit Opcode field.

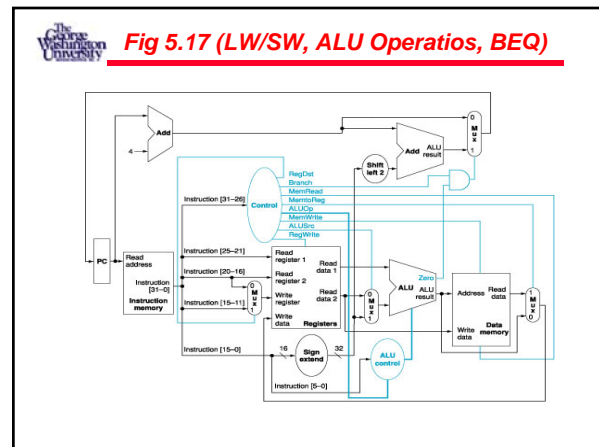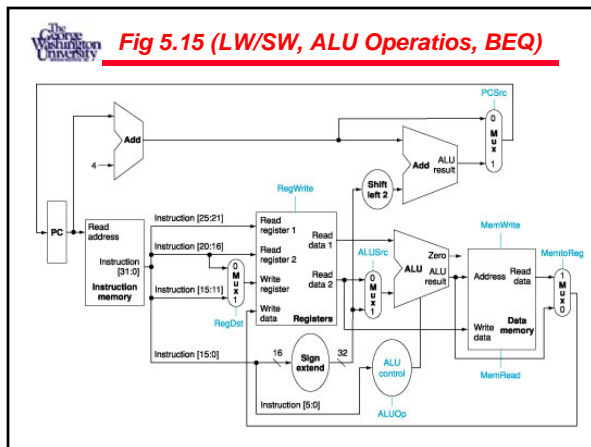

Control Signals

inst	Register Transfer
ADD	$R[rd] \leftarrow R[rs] + R[rt]; \quad PC \leftarrow PC + 4$ ALUSrc = RegB, ALUctr = "add", RegDst = rd, RegWr, nPC_sel = "+4"
SUB	$R[rd] \leftarrow R[rs] - R[rt]; \quad PC \leftarrow PC + 4$ ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __
Ori	$R[rt] \leftarrow R[rs] + \text{zero_ext}(Imm16); \quad PC \leftarrow PC + 4$ ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __
LOAD	$R[rt] \leftarrow MEM[R[rs] + \text{sign_ext}(Imm16)]; \quad PC \leftarrow PC + 4$ ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __
STORE	$MEM[R[rs] + \text{sign_ext}(Imm16)] \leftarrow R[rs]; \quad PC \leftarrow PC + 4$ ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __
BEQ	if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(Imm16) \parallel 00$ else $PC \leftarrow PC + 4$ ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __

Control Signals (Answer)



inst	Register Transfer
ADD	$R[rd] \leftarrow R[rs] + R[rt]; \quad PC \leftarrow PC + 4$ ALUSrc = RegB, ALUctr = "add", RegDst = rd, RegWr, nPC_sel = "+4"
SUB	$R[rd] \leftarrow R[rs] - R[rt]; \quad PC \leftarrow PC + 4$ ALUSrc = RegB, ALUctr = "sub", RegDst = rd, RegWr, nPC_sel = "+4"
Ori	$R[rt] \leftarrow R[rs] + \text{zero_ext}(Imm16); \quad PC \leftarrow PC + 4$ ALUSrc = Im, Extop = "Z", ALUctr = "or", RegDst = rt, RegWr, nPC_sel = "+4"
LOAD	$R[rt] \leftarrow MEM[R[rs] + \text{sign_ext}(Imm16)]; \quad PC \leftarrow PC + 4$ ALUSrc = Im, Extop = "Sn", ALUctr = "add", MemtoReg, RegDst = rt, RegWr, nPC_sel = "+4"
STORE	$MEM[R[rs] + \text{sign_ext}(Imm16)] \leftarrow R[rs]; \quad PC \leftarrow PC + 4$ ALUSrc = Im, Extop = "Sn", ALUctr = "add", MemWr, nPC_sel = "+4"
BEQ	if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(Imm16) \parallel 00$ else $PC \leftarrow PC + 4$ nPC_sel = EQUAL, ALUctr = "sub"







Step 5: Logic for each control signal

- ◆ nPC_sel <= if (OP == BEQ) then EQUAL else 0
- ◆ ALUSrc <= if (OP == "000000") then "regB" else "immed"
- ◆ ALUctr <= if (OP == "000000") then funct
 elseif (OP == Ori) then "OR"
 elseif (OP == BEQ) then "sub"
 else "add"
- ◆ ExtOp <= _____
- ◆ MemWr <= _____
- ◆ MemtoReg <= _____
- ◆ RegWr: <= _____
- ◆ RegDst: <= _____

Step 5: Logic for each control signal (Answer)

- ◆ nPC_sel <= if (OP == BEQ) then EQUAL else 0
- ◆ ALUSrc <= if (OP == "000000") then "regB" else "immed"
- ◆ ALUctr <= if (OP == "000000") then funct
 elseif (OP == Ori) then "OR"
 elseif (OP == BEQ) then "sub"
 else "add"
- ◆ ExtOp <= if (OP == Ori) then "zero" else "sign"
- ◆ MemWr <= (OP == Store)
- ◆ MemtoReg <= (OP == Load)
- ◆ RegWr: <= if ((OP == Store) || (OP == BEQ)) then 0 else 1
- ◆ RegDst: <= if ((OP == Load) || (OP == Ori)) then 0 else 1

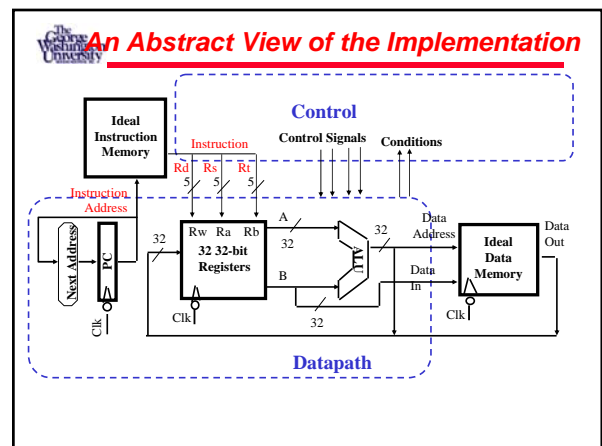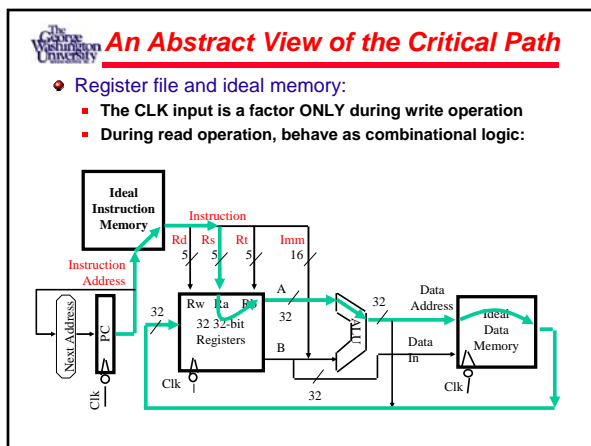

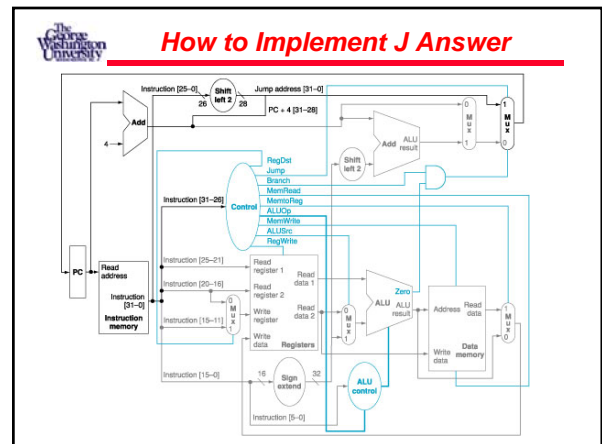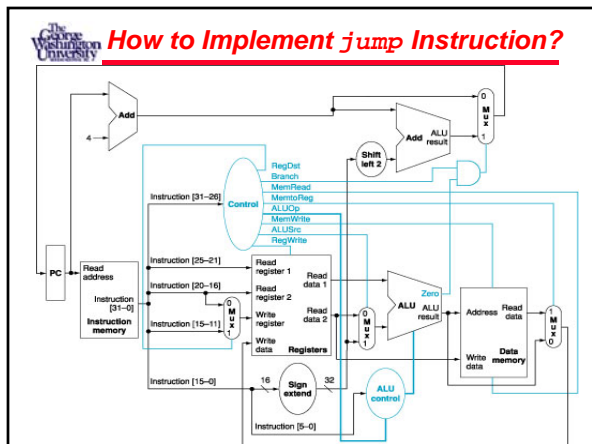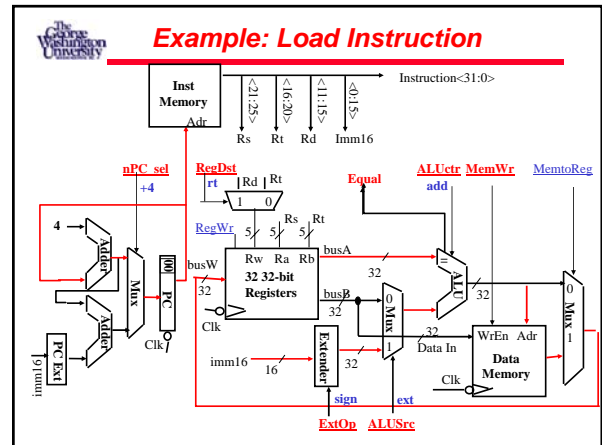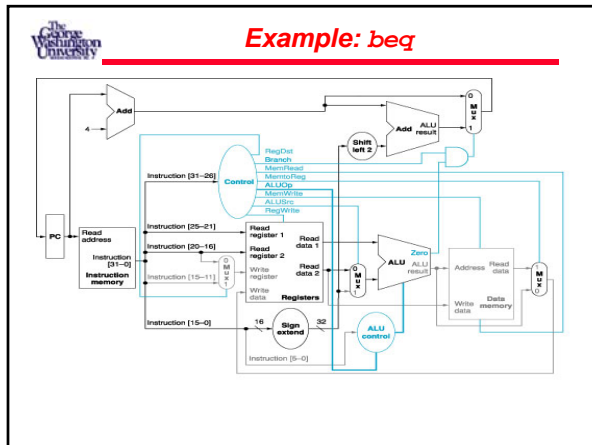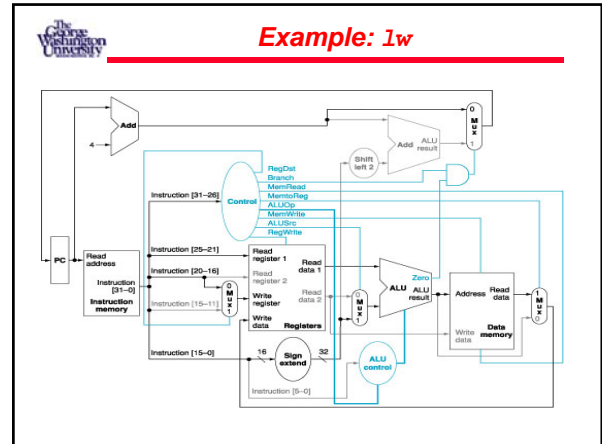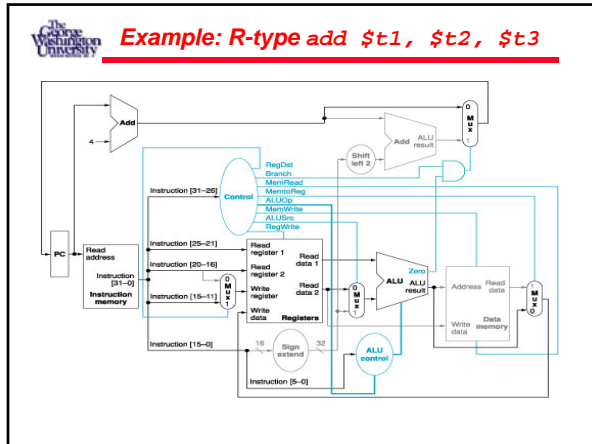



Performance of Single-Cycle Datapath

- **Time needs by functional units:**
 - Memory units: 200 ps
 - ALU and adders: 100 ps
 - Register file (r/w): 50 ps
 - No delay for other units
- **Two single cycle datapath implementations**
 - Clock cycle time is the same for all instructions
 - Variable clock cycle time per instruction
- **Instruction mix: 25% loads, 10% stores, 45% ALU, 15% branches, and 5% jumps**
- **Compare the performance of R-type, lw, sw, branch, and j**
- **Answer can be found at page 315-316**



Single-Cycle Processor

- **Advantage**
 - One clock cycle per instruction
- **Disadvantage**
 - Clock cycle is long



Summary

- **5 steps to design a processor**
 1. Analyze instruction set => datapath requirements
 2. Select set of datapath components & establish clock methodology
 3. Assemble datapath meeting the requirements
 4. Analyze implementation of each instruction to determine setting of control points that affects the register transfer
 5. Assemble the control logic
- **MIPS makes it easier**
 - Instructions same size
 - Source registers always in same place
 - Immediates same size, location
 - Operations always on registers/immediates
- **Single cycle datapath => CPI=1, CCT => long**