

Name: _____

Lab Section: _____

ECE 2140
Experiment 11 Prelab
Programmable Logic Devices
4-Input Multiplexer

1. **Read through Experiment 11.**
2. Look up the data sheets for the parts used in the experiment.
 - a. Find the following specifications for each IC

Recommended (Nominal) Operating Voltages	
	GAL16V8
V_{CC}	
V_{IL}	
V_{IH}	
V_{OL}	
V_{OH}	

3. A 4-input multiplexer can be made using three 2-input MUXs. Draw a schematic for this: