

Name: _____

Lab Section: _____

ECE 2140


Experiment 8 Prelab

Seven Segment Decoder

1. Read through Experiment 8.

2. Look up the data sheets for the parts used in the experiment.

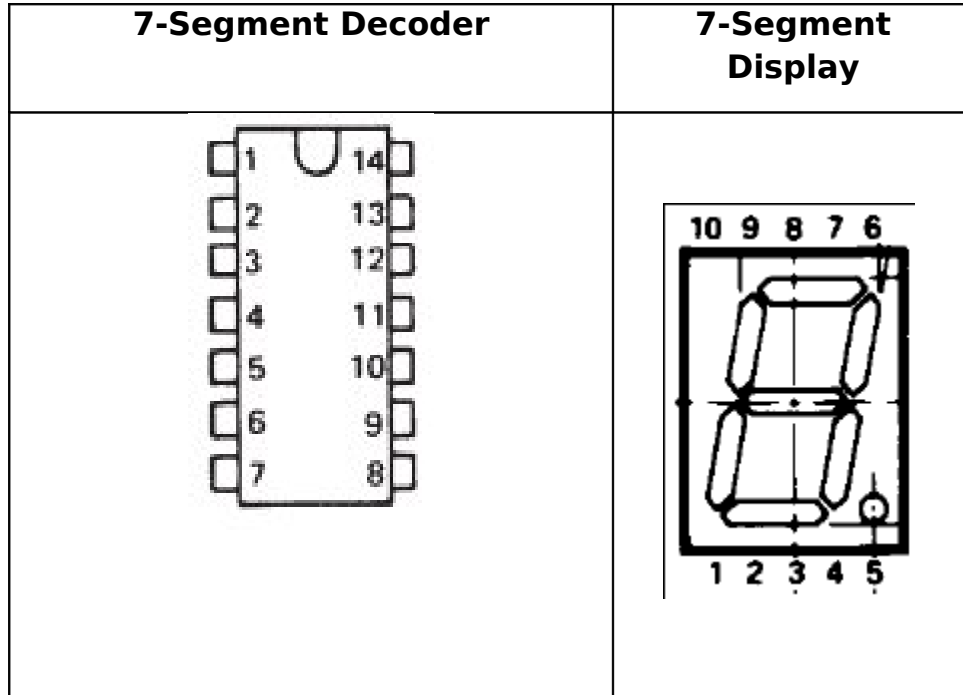a. Label all pins according to the data sheet:



b. Find the following specifications for each IC:

Recommended (Nominal) Operating Voltages	
	7-Seg Decoder
V_{CC}	
V_{IL}	
V_{IH}	
V_{OL}	
V_{OH}	

Name: _____

Lab Section: _____

3. Fill out the truth table

Find out how a 7-segment decoder operates from the data sheet, and fill out the following truth table:

Input	Output (a b c d e f g)
0000	
0001	
0010	
0011	
0100	
0101	
0110	
0111	
1000	
1001	

4. Draw a schematic for the experiment:

5. (Extra Credit - submit at beginning of lab) Derive your own 7-segment decoder. Show all work.