

Name: _____

Lab Section: _____

ECE 2140
Experiment 10 Prelab
Programmable Logic Devices
Half Adder

Modified for Spring 2012

1. Read through Experiment 10.

2. Look up the data sheets for the parts used in the experiment.

- a. Find the following specifications for each IC. Do not worry about the pin layout for this chip yet; we will discuss that in lab.

Recommended (Nominal) Operating Voltages	
GAL16V8	
V_{CC}	
V_{IL}	
V_{IH}	
V_{OL}	
V_{OH}	

3. Find the simplified Boolean expressions for the Sum and Carry outputs:

X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

4. Draw the gate-level schematic for these 2 Boolean expressions: