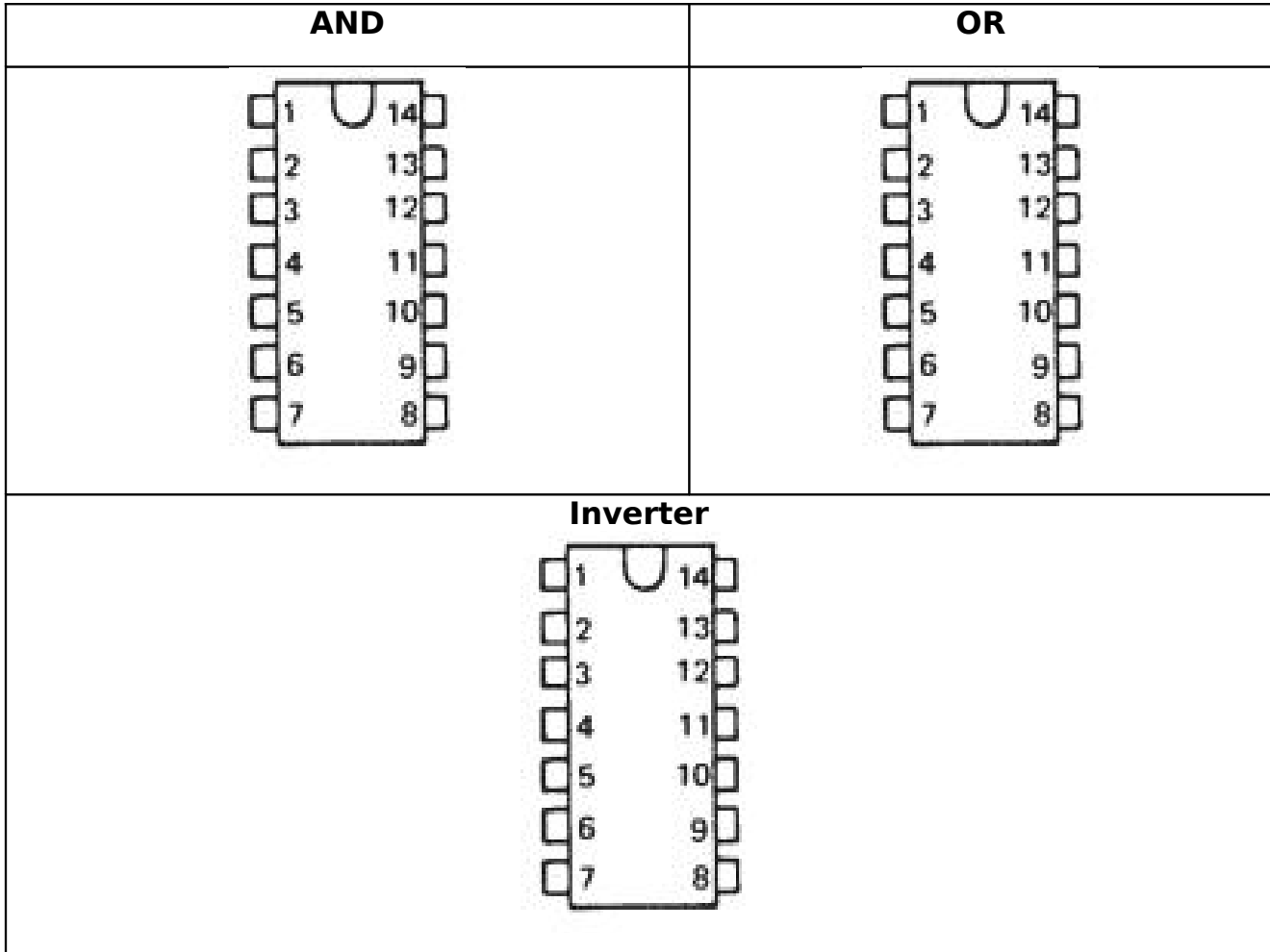


Name: _____

Lab Section: _____

ECE 2140
 Experiments 5 & 6 Prelab
 Sum-of-Products & Product of Sums Realization

1. Read through Experiment 5.
2. Look up the data sheets for the AND, OR, and Inverter gate ICs.
 - a. Label all pins according to the data sheet:



- b. Find the following specifications for each IC:

Absolute Maximum Voltages			
	AND	OR	Inverter
V_{CC}			
Input voltage			

Name: _____ Lab Section: _____

Recommended (Nominal) Operating Voltages			
	AND	OR	Inverter
V_{CC}			
V_{IL}			
V_{IH}			
V_{OL}			
V_{OH}			

3. Find the **sum-of-product** canonical expression from **Part 2** of **Experiment 5**:

X	Y	f (output)
0	0	0
0	1	1
1	0	1
1	1	0

4. Draw a schematic for **Experiment 5**. Make sure you show where the function generator, oscilloscope, and DMM are connected (if necessary).

Part 3:

Name: _____

Lab Section: _____

5. Find the ***product-of-sum*** canonical expression from **Part 2** of **Experiment 6**:

X	Y	f (output)
0	0	0
0	1	1
1	0	1
1	1	0

6. Draw a schematic for **Experiment 6**. Make sure you show where the function generator, oscilloscope, and DMM are connected (if necessary).

Part 3: