

# Optimizing Power Transfer to a Load Using Matlab


S. Ahmadi, T. Tag and T. Farmer

- **Problem Description**

The aim of this task is to calculate the maximum power transferred from a fixed supply, to a load.

To put this requirement into perspective, *given a fixed supply, i.e. an electrical outlet, what is the maximum load you can connect to it in order to obtain the maximum power transfer from the supply to the load.*

As shown in the Figure below, the supply can be represented by two components, a voltage source, denoted by  $V_s$ , and a supply resistance, denoted by  $R_s$ . The load being applied can be simplified to its equivalent total resistance,  $R_L$ . By continually varying this load, and calculating the corresponding power at each value, the load that results in maximum power can be obtained.

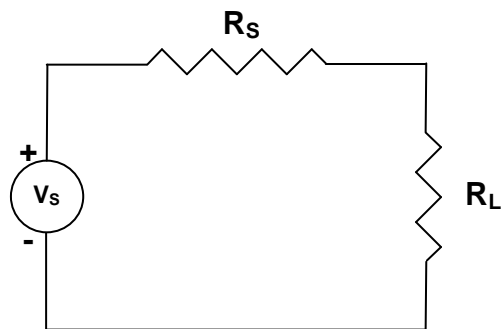

**Figure 1:** Circuit under test.

In order to be able to solve this sort of problem the following equation can be used:

$$\text{Power} = \left( \frac{V_s}{R_s + R_L} \right)^2 * R_L$$

Using MATLAB, carry out the following:

- 1) Given a supply, with  $V_S = 6V$  and  $R_S = 330\Omega$ , vary the load resistance,  $R_L$ , between  $50\Omega$  and  $500\Omega$  in increments of  $5\Omega$ , and plot Power  $P$  vs  $R_L$ . From this graph, extract the value of  $R_L$  which gives maximum power.  
(*HINT: we do not want  $\max(P)$ , we want the  $R_L$  that causes the  $\max(P)$ .*)  
(*NOTE: you cannot use the graph to determine the value of  $R_L$ , you must use matlab commands to find it*)
- 2) Again plot Power  $P$  vs  $R_L$ , but this time use supply values:  $V_S = 6V$ ,  $R_S = 500\Omega$ . Vary  $R_L$ , in increments of  $10\Omega$ , between  $300\Omega$  and  $700\Omega$ . Extract the value of the load resistance,  $R_L$ , such that maximum power is obtained.  
(*HINT: we do not want  $\max(P)$ , we want the  $R_L$  that causes the  $\max(P)$ .*)  
(*NOTE: you cannot use the graph to determine the value of  $R_L$ , you must use matlab commands to find it*)
- 3) From your results, what is the relationship, if any, between the supply resistance, and the load resistance, in order to obtain maximum power?

- ***Deriving the Equation:***

The two main equations that are used are Ohms Law, and the power equation:

$$\text{Ohms Law: } V = IR$$

$$\text{Power Equation: } P = IV = I^2R.$$

where  $V = \text{Voltage}$

$I = \text{Current}$

$R = \text{Resistance}$

First we must calculate the current running through the circuit of **Figure 1**. Therefore, using Ohms Law, and the rule of resistances in series, we get:

$$I = \left( \frac{V_S}{R_S + R_L} \right)$$

Substituting this into our power equation, we get:

$$P = \left( \frac{V_S}{R_S + R_L} \right)^2 * R$$

The  $R$  at the end of this equation represents the resistance of the load that we are connecting to our circuit, i.e.  $R_L$ . By substituting into the above equation accordingly:

$$P = \left( \frac{V_S}{R_S + R_L} \right)^2 * R_L$$